



C16-EC-303

6234

**BOARD DIPLOMA EXAMINATION, (C-16)
AUGUST/SEPTEMBER—2021
DECE - THIRD SEMESTER EXAMINATION
DIGITAL ELECTRONICS**

Time : 3 hours]

[Total Marks : 80

PART—A

3×10=30

- Instructions :**
- (1) Answer **all** questions.
 - (2) Each question carries **three** marks.
 - (3) Answers should be brief and straight to the point and shall not exceed five simple sentences.

1. Convert $(110101.100)_2$ into decimal, octal and hexadecimal numbers.
2. Compare weighted and unweighted codes.
3. State De-Morgan's theorems.
4. Define the terms propagation delay and noise margin of digital ICs.
5. Realize half-adder circuit using NAND gates only.
6. State the need for a tri-state buffer.
7. Draw the symbols of edge triggered D and T flip-flops.
8. Distinguish between synchronous and asynchronous counters.
9. Draw the circuit of 4-bit ring counter.
10. Compare static RAM and dynamic RAM.

*

PART—B

- Instructions :** (1) Answer *any five* questions.
(2) Each question carries **ten** marks.
(3) Answers should be comprehensive and criterion for valuation is the content but not the length of the answer.

- 11.** Explain the working of Universal logic gates (NAND, NOR gates) with truth tables. 10
- 12.** (a) Simplify the Boolean expression $Y(\bar{A}, \bar{B}, \bar{C}) = \bar{A}BC + A\bar{B}C + ABC\bar{C} + ABC$ using K-map. 6
(b) Write the gray code for binary number 11010101. 4
- 13.** Draw and explain the working of TTL NAND gate with totem pole output. 5+5
- 14.** Draw and explain the logic circuit of 4×1 multiplexer. 5+5
- 15.** Explain the operation of full-adder circuit with truth table using basic gates. 10
- 16.** (a) Explain the working of level clocked J-K flip-flop with circuit diagram and truth table. 7
(b) What is race around condition? 3
- 17.** Draw and explain the working of asynchronous decade counter with timing diagram. 10
- 18.** Draw and explain the working of 4-bit shift left register with timing diagram. 10

*

★ ★ ★

*