

UNIT - II

Transmission Lines - II

Input Impedance Relations :-

Consider, a transmission line of length (l) terminated by a load impedance (Z_R) is shown in fig:

From fig: V_S - voltage source

Z_0 - characteristic impedance of transmission line

Z_{in} - input impedance of given Tx line
i.e. $Z_{in} = \frac{V_S}{I_S}$

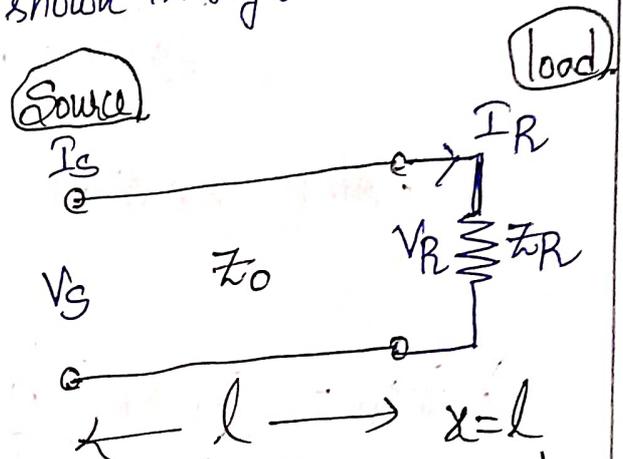


fig: Tx line with load from sending end

→ The voltage and current expressions at any distance (x) are in terms of V_R and I_R as:

$$\begin{aligned}
 V &= V_R \cosh p(l-x) + I_R Z_0 \sinh p(l-x) \\
 I &= I_R \cosh p(l-x) + \frac{V_R}{Z_0} \sinh p(l-x)
 \end{aligned}$$

At sending/source end: $x=0 ; V=V_S ; I=I_S$

• substituting these conditions in above expressions, we get

$$\begin{aligned}
 V_S &= V_R \cosh pl + I_R Z_0 \sinh pl \\
 I_S &= I_R \cosh pl + \frac{V_R}{Z_0} \sinh pl
 \end{aligned}$$

∴ input impedance $Z_{in} = \frac{V_S}{I_S} = \frac{V_R \cosh pl + I_R Z_0 \sinh pl}{I_R \cosh pl + \frac{V_R}{Z_0} \sinh pl}$

multiplying both Numerator & denominator by $\frac{z_0}{I_R}$,
we get:

$$z_{in} = \frac{\frac{z_0 V_R}{I_R} \cosh pl + \frac{I_R z_0}{I_R} \frac{z_0}{I_R} \sinh pl}{\frac{z_0 I_R}{I_R} \cosh pl + \frac{V_R}{z_0} \frac{z_0}{I_R} \sinh pl}$$

• Also substitute $z_R = \frac{V_R}{I_R}$ (load/termination impedance)

$$\Rightarrow z_{in} = \frac{z_0 z_R \cosh pl + z_0^2 \sinh pl}{z_0 \cosh pl + z_R \sinh pl}$$

$$\therefore z_{in} = z_0 \left[\frac{z_R \cosh pl + z_0 \sinh pl}{z_0 \cosh pl + z_R \sinh pl} \right] \Rightarrow \text{Input impedance of a Tx Line having length } (l) \text{ \& characteristic impedance } (z_0).$$

Simplification:

Further simplify the above z_{in} expression by dividing both numerator & denominator by $\cosh pl$.

$$z_{in} = z_0 \left[\frac{z_R \frac{\cosh pl}{\cosh pl} + z_0 \frac{\sinh pl}{\cosh pl}}{z_0 \frac{\cosh pl}{\cosh pl} + z_R \frac{\sinh pl}{\cosh pl}} \right]$$

$$\Rightarrow z_{in} = z_0 \left[\frac{z_R + z_0 \tanh pl}{z_0 + z_R \tanh pl} \right] \Rightarrow \text{simplified expression of } z_{in}.$$

→ By varying the load of the Tx line, there exists various special cases such as:

- ① short-circuited line ($Z_R = 0$)
- ② open-circuited line ($Z_R = \infty$)
- ③ Matched line ($Z_R = Z_0$)
- ④ Any other termination (Z_R)

① Short-circuited line :-

→ The short circuit is formed when the load impedance is characterized by zero value ($Z_R = 0$) since $V = 0$ for short circuit as shown in fig:

Let $Z_{sc} \rightarrow$ input impedance of the short-circuited Tx line.

i.e. $Z_{sc} = \frac{V_S}{I_S}$

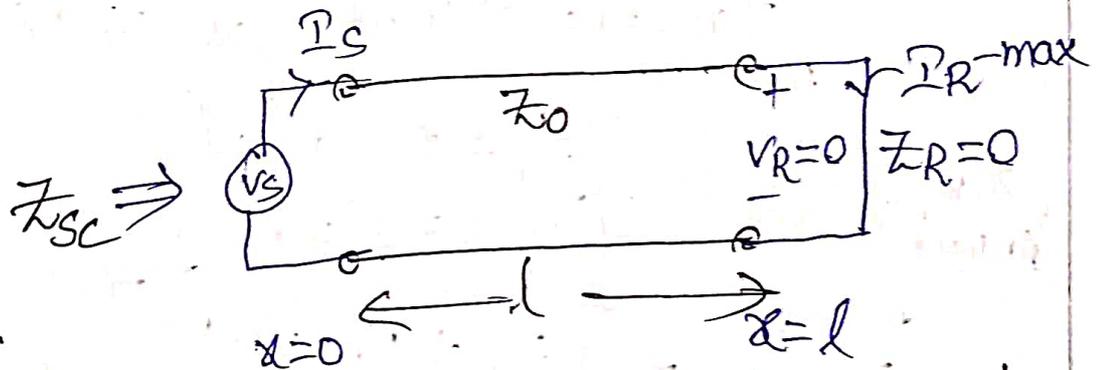


Fig: A short-circuited Tx line.

→ The voltage & current expressions at any distance 'x' from sending end in terms of V_S & I_S are:

$$V = V_S \cosh px - I_S Z_0 \sinh px \quad \text{--- ①}$$

$$I = I_S \cosh px - \frac{V_S}{Z_0} \sinh px$$

At $x=l$: $V=0$ substitute in eq ①

$$\therefore 0 = V_S \cosh \beta l - I_S Z_0 \sinh \beta l$$

$$\Rightarrow V_S \cosh \beta l = I_S Z_0 \sinh \beta l$$

$$\Rightarrow Z_{sc} = \frac{V_S}{I_S} = Z_0 \frac{\sinh \beta l}{\cosh \beta l} = Z_0 \tanh \beta l$$

$$\therefore \boxed{Z_{sc} = Z_0 \tanh \beta l} \text{ — input impedance of short-circuited Tx line.}$$

For lossless line: $\tanh \beta l = j \tan \beta l$

$$\therefore \boxed{Z_{sc} = j Z_0 \tan \beta l} \text{ — input impedance of short-circuited lossless Tx line.}$$

Another approach for Z_{sc} :

$$\text{As we know: } Z_{in} = Z_0 \left[\frac{Z_R + Z_0 \tanh \beta l}{Z_0 + Z_R \tanh \beta l} \right] \text{ — (A)}$$

Since load is short-circuited: $\boxed{Z_R = 0}$

Substituting in above Eqⁿ (A)

$$Z_{sc} = Z_0 \left[\frac{Z_0 \tanh \beta l}{Z_0} \right] = Z_0 \tanh \beta l$$


$$\therefore \boxed{Z_{sc} = Z_0 \tanh \beta l}$$

Similarly, for lossless line:

$$\boxed{Z_{sc} = j Z_0 \tan \beta l}$$

② Open-Circuited Line :-

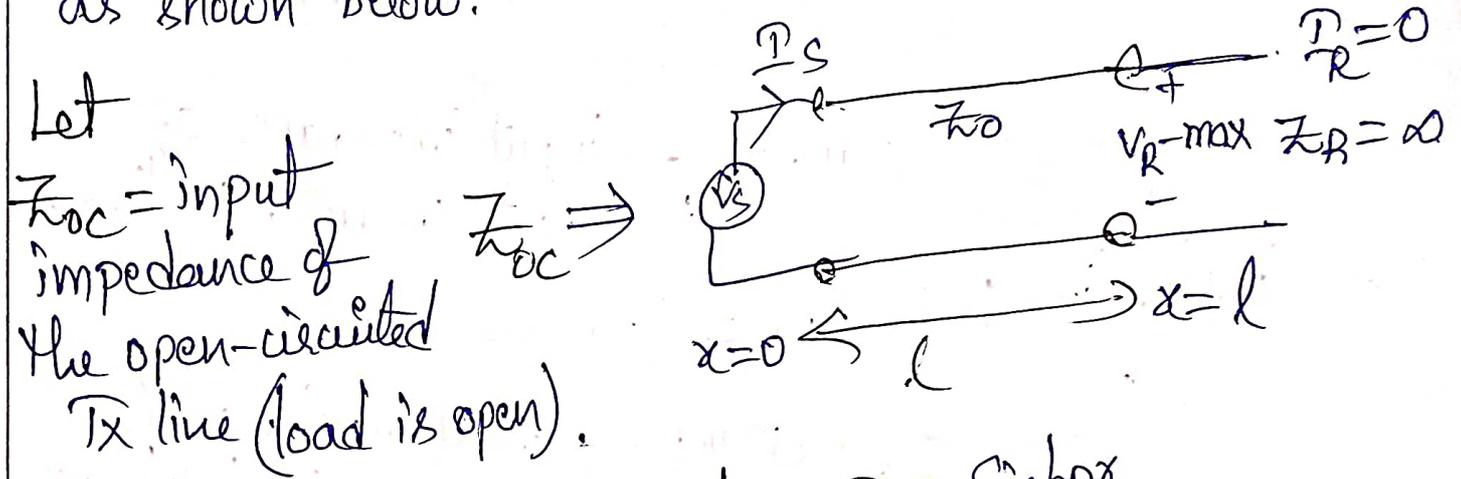→ An open-circuited line is formed when the load impedance has infinite value ($Z_R = \infty$) since $I = 0$ for open circuit as shown below:



We know :

$$V = V_s \cosh px - I_s Z_0 \sinh px$$

$$I = I_s \cosh px - \frac{V_s}{Z_0} \sinh px \quad \text{--- (2)}$$

At $x=l$: $I = 0$ substitute in Eqⁿ (2)

$$0 = I_s \cosh pl - \frac{V_s}{Z_0} \sinh pl$$

$$\Rightarrow \frac{V_s}{Z_0} \sinh pl = I_s \cosh pl$$

$$\therefore Z_{oc} = \frac{V_s}{I_s} = Z_0 \frac{\cosh pl}{\sinh pl} = Z_0 \coth pl$$

$$\boxed{Z_{oc} = Z_0 \coth pl} \quad \text{--- Input impedance of open-circuited Tx line}$$

For lossless line: $\tanh pl = j \tan pl$

$$Z_{oc} = \frac{Z_0}{\tanh pl} = \frac{Z_0}{j \tan pl} = -j Z_0 \cot pl$$

$$\therefore \boxed{Z_{oc} = -j Z_0 \cot pl} \quad \text{--- Input impedance of OC lossless Tx line}$$

Another approach of Z_{oc} :

As we know: $Z_{in} = Z_0 \left[\frac{Z_R + Z_0 \tanh \beta l}{Z_0 + Z_R \tanh \beta l} \right]$

Since load is open-circuited: $Z_R = \infty$

• on substitution:

$$Z_{oc} = Z_{in} = Z_0 \left[\frac{1 + \frac{Z_0 \cancel{\tanh \beta l}}{\cancel{Z_R}}}{\frac{Z_0}{\cancel{Z_R}} + \tanh \beta l} \right]$$

(dividing both Nr & Dr by Z_R)

$$= \frac{Z_0}{\tanh \beta l} = Z_0 \coth \beta l$$

$$\therefore Z_{oc} = Z_0 \coth \beta l$$

Similarly, for lossless line $Z_{oc} = -j Z_0 \cot \beta l$

Important Relations:

$$\begin{aligned} \textcircled{1} \quad Z_{sc} \times Z_{oc} &= Z_0 \tanh \beta l \times Z_0 \coth \beta l \\ &= Z_0 \tanh \beta l \times Z_0 \frac{1}{\tanh \beta l} = Z_0^2 \end{aligned}$$

$$\therefore Z_0 = \sqrt{Z_{oc} Z_{sc}}$$

$$\textcircled{2} \quad \frac{Z_{sc}}{Z_{oc}} = \frac{Z_0 \tanh \beta l}{Z_0 \coth \beta l} = \tanh^2 \beta l$$

$$\therefore \tanh \beta l = \sqrt{\frac{Z_{sc}}{Z_{oc}}}$$

③ Matched line

When the Tx line is terminated by the characteristic impedance, the load of the line is equal to characteristic impedance ($Z_R = Z_0$) and it is called as matched line.

→ As we know: $Z_{in} = Z_0 \left[\frac{Z_R + Z_0 \tanh \beta l}{Z_0 + Z_R \tanh \beta l} \right]$

Substituting the condition: $Z_R = Z_0$

$$Z_{in} = Z_0 \left[\frac{Z_0 + Z_0 \tanh \beta l}{Z_0 + Z_0 \tanh \beta l} \right] = Z_0$$

∴ $Z_{in} = Z_0$ i.e. input impedance is equal to characteristic impedance for a matched line.

Note :- Totally there are 4 types of terminations. They are ① Short ckt ② open ckt ③ with Z_0 ④ Any other

① Short ckt ($Z_R = 0$): If the line is terminated with shorted load then total reflection of energy takes place.

② Open ckt ($Z_R = \infty$): If the line is terminated with open load then total reflection of energy takes place.

③ Matched termination ($Z_R = Z_0$): If the line is terminated with Z_0 (characteristic impedance), there is no reflection of energy.

④ Any other termination: If the line is terminated with Z_R then there is a partial reflection.

Input Impedance Relations for lossless Tx line :-

→ For lossless Tx line : $\alpha = 0$

$$P = j\beta$$

(since $p = \alpha + j\beta$)

Let, consider the term:

$$\tanh p l = \tanh(j\beta l) = j \tan \beta l \quad (\text{since } \tanh(jx) = j \tan x)$$

$$\therefore \boxed{\tanh p l = j \tan \beta l} \rightarrow \text{for lossless line}$$

① Input impedance :-

As we know: $Z_{in} = Z_0 \left[\frac{Z_R + Z_0 \tanh p l}{Z_0 + Z_R \tanh p l} \right]$

$$\therefore \boxed{Z_{in} = Z_0 \left[\frac{Z_R + j Z_0 \tan \beta l}{Z_0 + j Z_R \tan \beta l} \right]}$$

② Input impedance under short-circuit load :-

As we know: $Z_{sc} = Z_0 \tanh p l$

$$\therefore \boxed{Z_{sc} = j Z_0 \tan \beta l}$$

③ Input impedance under open-circuit load :-

As we know: $Z_{oc} = Z_0 \coth p l$

$$= \frac{Z_0}{\tanh p l} = \frac{Z_0}{j \tan \beta l}$$

$$\therefore \boxed{Z_{oc} = -j Z_0 \cot \beta l}$$

④ Input impedance under matched load: $Z_{in} = Z_0$

Short-circuit (sc) and open-circuit (oc) lines:-

Consider, the fig: shows the variations of Z_{oc} and Z_{sc} as a function of the physical length (or) electrical length of the Tx lines.

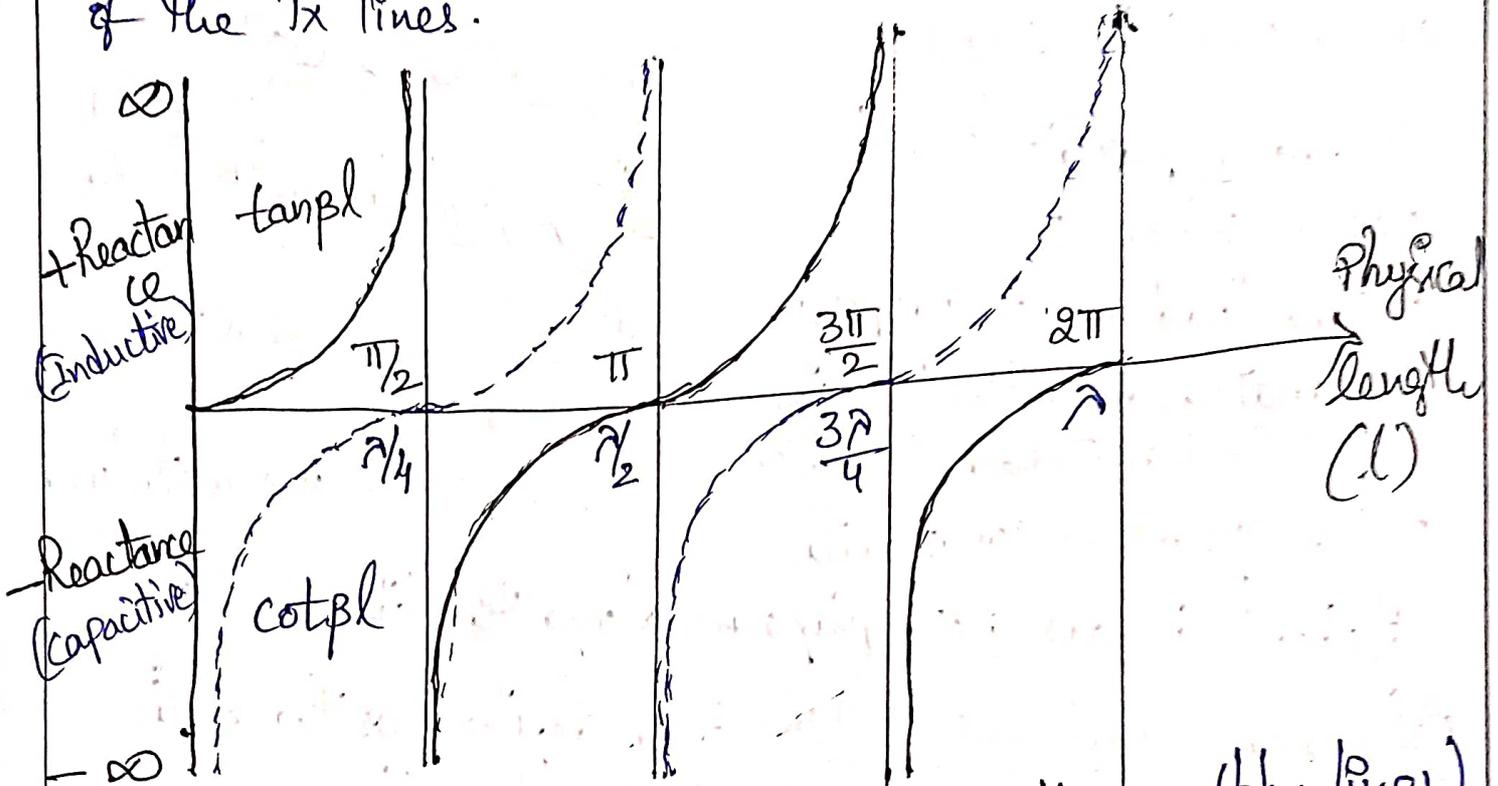


fig: variations of the input impedance with Z_{oc} (blue lines) & Z_{sc} (black lines).

① Consider the variation of Z_{sc} only:-

(i) At even multiples of $\pi/4$:

The line offers zero reactance \Rightarrow behaves like series resonant circuit.

(ii) At odd multiples of $\pi/4$:

The line offers infinite reactance \Rightarrow behaves as a parallel resonant circuit.

② Consider the variation of Z_{oc} only:-

(i) At even multiples of $\pi/4$:


The line offers infinite reactance \Rightarrow behaves as parallel resonant circuit.

(ii) At odd multiples of $\pi/4$:

The line offers zero reactance \Rightarrow behaves as series resonant circuit.

Reflection Coefficient:-

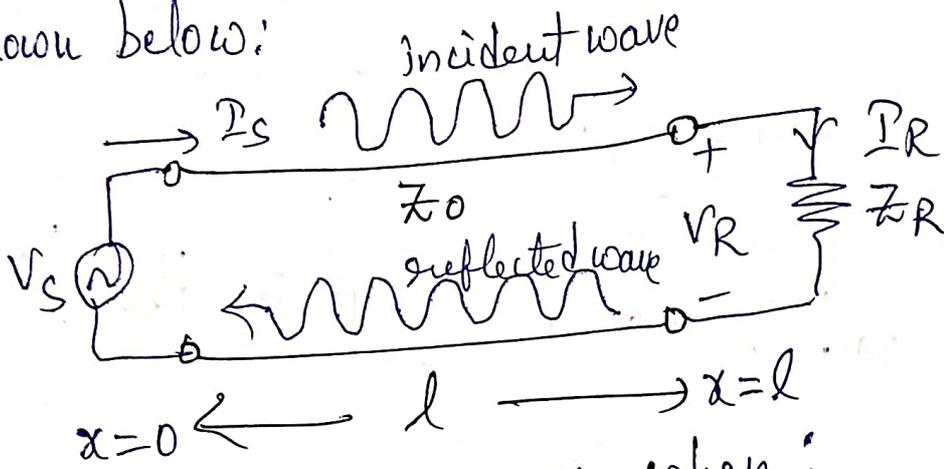→ Consider, a Tx line of length l , having characteristic impedance (Z_0) is connected with source & load (Z_R) as shown below:



→ The reflection may occur when:

- ① The load is not properly matched to the Tx line (Mismatched load)
- ② The primary constants (R, L, C, G) are not uniformly distributed along the length of line.

Definition:- The reflection coefficient is defined as the ratio of reflected voltage to the incident voltage
(or) -ve ratio of reflected current to incident current.

$$\text{i.e. } \Gamma = \frac{V_R}{V_i} = -\frac{I_R}{I_i}$$

Derivation:- Consider the voltage & current expressions

$$\text{as: } V = A \cosh px + B \sinh px$$

$$I = -\frac{1}{Z_0} (A \sinh px + B \cosh px)$$

• Replace sine & cosine terms using exponentials such as:

$$V = ae^{Px} + be^{-Px}$$

$$I = \frac{-1}{Z_0} (ae^{Px} - be^{-Px})$$

where e^{-Px} term represents forward travelling wave
 e^{Px} term represents reflected wave.

Assume!: Load is placed at $y=0$ then $x=-y$

\therefore V & I expressions are rewrite as

$$V = ae^{-Py} + be^{Py}$$

$$I = \frac{-1}{Z_0} (ae^{-Py} - be^{Py})$$

where,
 e^{Py} - forward wave
 e^{-Py} - reflected wave.

\therefore reflection coefficient $(\Gamma) = \frac{ae^{-Py}}{be^{Py}} = \frac{a}{b} e^{-2Py}$

$\therefore \Gamma = \frac{a}{b} e^{-2Py}$ → expression of reflection coefficient at a distance (y) from load end.

determine constants $(a \& b)$:-

Let: Load conditions: $y=0 ; V=V_R ; I=I_R$

substitute in above expressions:

$V_R = a + b$ — (1)

$I_R = \frac{-1}{Z_0} (a - b) = \frac{1}{Z_0} (b - a) \Rightarrow I_R Z_0 = b - a$ — (2)

(1) + (2) $\Rightarrow b = \frac{V_R + I_R Z_0}{2}$

$$\textcircled{1} - \textcircled{2} \Rightarrow \boxed{a = \frac{V_R - I_R Z_0}{2}}$$

\therefore At load ($y=0$):-

$$\text{Reflection coefficient } (\Gamma_L) = \frac{a}{b} e^{-2p(0)} = \frac{a}{b}$$

$$\Rightarrow \Gamma_L = \frac{\left(\frac{V_R - I_R Z_0}{2}\right)}{\left(\frac{V_R + I_R Z_0}{2}\right)} = \frac{V_R - I_R Z_0}{V_R + I_R Z_0} = \frac{\frac{V_R}{I_R} - Z_0}{\frac{V_R}{I_R} + Z_0}$$

$$\therefore \boxed{\Gamma_L = \frac{Z_R - Z_0}{Z_R + Z_0}} \quad \left(\text{since } \frac{V_R}{I_R} = Z_R\right)$$

reflection coefficient of load in terms of impedances.

various load conditions:-

① short-circuited load: $Z_R = 0$ then $\Gamma_L = \frac{-Z_0}{Z_0} = -1$
 $\therefore \boxed{\Gamma_L = -1} \rightarrow$ Maximum reflections with 180° phase shift

② open-circuited load: $Z_R = \infty$ then $\Gamma_L = \frac{1 - Z_0/Z_R}{1 + Z_0/Z_R} = \frac{1 - 0}{1 + 0} = 1$
 $\therefore \boxed{\Gamma_L = 1} \rightarrow$ Maximum reflections with same phase.

③ Matched load: $Z_R = Z_0$ then $\Gamma_L = \frac{Z_0 - Z_0}{Z_0 + Z_0} = 0$.

$\boxed{\Gamma_L = 0} \rightarrow$ No reflections.

Note:- The range of reflection coefficient: $\boxed{0 \text{ to } 1}$

Input impedance in terms of reflection coefficient

We know that: $Z_{in} = Z_0 \left[\frac{Z_R \cosh \beta l + Z_0 \sinh \beta l}{Z_0 \cosh \beta l + Z_R \sinh \beta l} \right]$

$$= Z_0 \left[\frac{Z_R \left(\frac{e^{\beta l} + e^{-\beta l}}{2} \right) + Z_0 \left(\frac{e^{\beta l} - e^{-\beta l}}{2} \right)}{Z_0 \left(\frac{e^{\beta l} + e^{-\beta l}}{2} \right) + Z_R \left(\frac{e^{\beta l} - e^{-\beta l}}{2} \right)} \right]$$

$$= Z_0 \left[\frac{(Z_R + Z_0) e^{\beta l} + (Z_R - Z_0) e^{-\beta l}}{(Z_R + Z_0) e^{\beta l} - (Z_R - Z_0) e^{-\beta l}} \right]$$

divide Nr & Dr by $(Z_R + Z_0) e^{\beta l}$

$$= Z_0 \left[\frac{1 + \left(\frac{Z_R - Z_0}{Z_R + Z_0} \right) e^{-2\beta l}}{1 - \left(\frac{Z_R - Z_0}{Z_R + Z_0} \right) e^{-2\beta l}} \right]$$

$$= Z_0 \left[\frac{1 + \Gamma_l e^{-2\beta l}}{1 - \Gamma_l e^{-2\beta l}} \right] \quad \left(\text{since } \Gamma_l = \frac{Z_R - Z_0}{Z_R + Z_0} \right)$$

$$\therefore Z_{in} = Z_0 \left[\frac{1 + \Gamma_l e^{-2\beta l}}{1 - \Gamma_l e^{-2\beta l}} \right]$$

input impedance in terms of reflection coefficient (Γ_l).

$\lambda/4$, $\lambda/2$ and $\lambda/8$ Lines :-


The input impedance of lossless transmission line

$$Z_{in} = Z_0 \left[\frac{Z_R + j Z_0 \tan \beta l}{Z_0 + j Z_R \tan \beta l} \right] ; \text{ where } \beta = \frac{2\pi}{\lambda}$$

$\lambda/4$ Line (Quarter wave transformer or Impedance transformer)

→ A Tx line of length $l = \lambda/4$ is called as Quarter wave transformer, used for "Impedance matching"
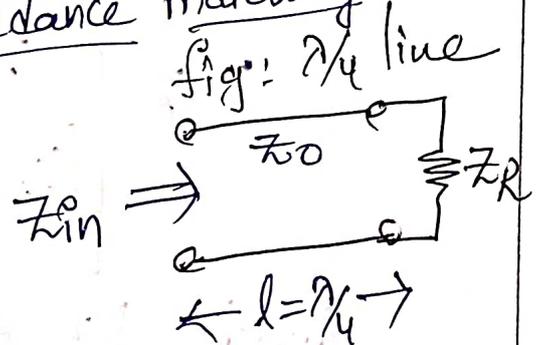
$$Z_{in} = Z_0 \left[\frac{Z_R + j Z_0 \tan\left(\frac{2\pi}{\lambda} \times \frac{\lambda}{4}\right)}{Z_0 + j Z_R \tan\left(\frac{2\pi}{\lambda} \times \frac{\lambda}{4}\right)} \right]$$



$$= Z_0 \left[\frac{Z_R + j Z_0 \tan \pi/2}{Z_0 + j Z_R \tan \pi/2} \right] = Z_0 \left[\frac{\frac{Z_R}{\tan \pi/2} + j Z_0}{Z_0 + j Z_R \frac{Z_0}{\tan \pi/2}} \right]$$

$$= Z_0 \left[\frac{j Z_0}{j Z_R} \right] = \frac{Z_0^2}{Z_R} \quad (\text{since } \tan \pi/2 = \infty)$$

$$\therefore Z_{in} = \frac{Z_0^2}{Z_R} \Rightarrow \boxed{Z_0 = \sqrt{Z_{in} Z_R}}$$

Various load conditions

- ① sc load: if $Z_R = 0 \Rightarrow Z_{in} = \infty$ (open circuited)
 - ② oc load: if $Z_R = \infty \Rightarrow Z_{in} = 0$ (short circuited)
 - ③ Inductive load: if $Z_R = jX \Rightarrow Z_{in} = -jX$ (capacitive)
 - ④ Capacitive load: if $Z_R = -jX \Rightarrow Z_{in} = jX$ (inductive)
- it transforms short into open & vice-versa

∴ A quarter-wave impedance transformer is a Tx line of length one-quarter wavelength ($\lambda/4$), terminated with some known impedance (Z_R).

- It presents at its input the dual of the impedance with which it is terminated.

$\lambda/8$ Line :-

A Tx line of length $l = \lambda/8$ having characteristic impedance (Z_0) is terminated with load impedance (Z_R) is shown below:

$$Z_{in} = Z_0 \left[\frac{Z_R + jZ_0 \tan\left(\frac{2\pi}{\lambda} \cdot \frac{\lambda}{8}\right)}{Z_0 + jZ_R \tan\left(\frac{2\pi}{\lambda} \cdot \frac{\lambda}{8}\right)} \right]$$

$$= Z_0 \left[\frac{Z_R + jZ_0 \tan \pi/4}{Z_0 + jZ_R \tan \pi/4} \right]$$

$$Z_{in} = Z_0 \left[\frac{Z_R + jZ_0}{Z_0 + jZ_R} \right]$$


(since $\tan \pi/4 = 1$)

$$\rightarrow \text{Now, } |Z_{in}| = Z_0 \frac{\sqrt{Z_R^2 + Z_0^2}}{\sqrt{Z_0^2 + Z_R^2}} = Z_0$$

$$\therefore |Z_{in}| = Z_0$$

Note:- ① A $\lambda/8$ line can transform a real impedance into a complex impedance.

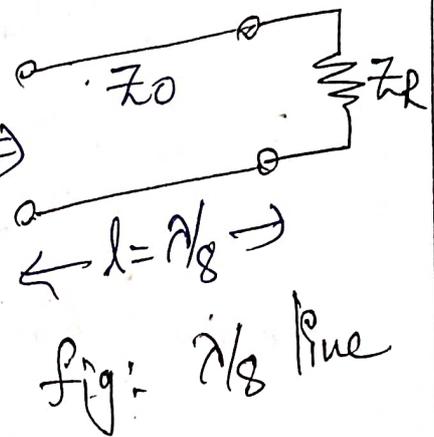② A $\lambda/4$ line can transform a real impedance into another real impedance.




$\lambda/2$ Line: A Tx line of length $[l = \lambda/2]$ having characteristic impedance (Z_0) is terminated with the load impedance (Z_R) is shown below:

$$Z_{in} = Z_0 \left[\frac{Z_R + jZ_0 \tan\left(\frac{2\pi}{\lambda} \times \lambda/2\right)}{Z_0 + jZ_R \tan\left(\frac{2\pi}{\lambda} \times \lambda/2\right)} \right]$$

$$= Z_0 \left[\frac{Z_R + jZ_0 \tan \pi}{Z_0 + jZ_R \tan \pi} \right]$$

$$= Z_0 \left[\frac{Z_R}{Z_0} \right] = Z_R$$

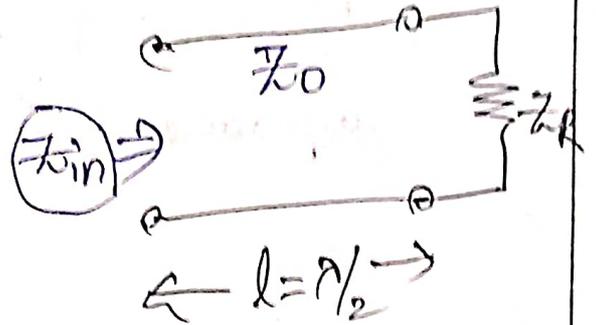\therefore $Z_{in} = Z_R \Rightarrow$ input impedance is equal to load impedance.



(since $\tan \pi = 0$)

Standing Waves in OC & SC Lines:-

→ A standing wave results from two waves (incident & reflected) travelling in opposite directions between the input end and the load end.

(i) At some points in the line, the 2 waves will always be in phase and will add.

∴ The places where 2 waves add will be points of maximum voltage, termed as anti-nodes.

(ii) At other points, the 2 waves will always be out of phase and will cancel.

∴ The points of cancellation will have minimum voltage, termed as nodes.

→ As the positions of maxima & minima (or) anti-nodes & nodes — voltage remain motionless, a standing wave is said to exist on the line.

① open-circuited lines:-


- At the open-end termination, there exist a
 - maximum voltage
 - minimum (zero) current

$$\therefore \boxed{Z = \infty}$$

Let quarter-wavelength ($l = \lambda/4$) from the open end,

• Incident wave will be 90° earlier

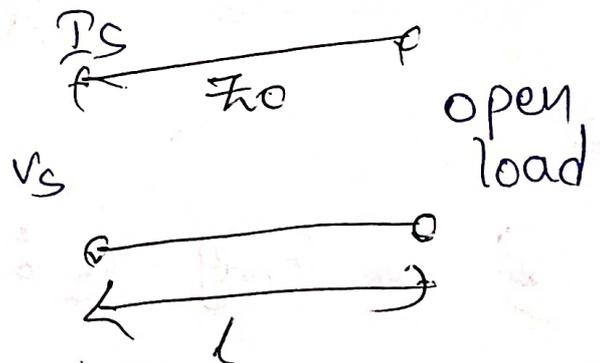• Reflected wave 90° later at the end, and



Thus both waves will be 180° out of phase.

\therefore At this point $\boxed{\text{voltage} = 0}$ (minimum) \Rightarrow current maximum occurs.

- Note:-
- ① Standing wave pattern repeated for every half-wave lengths.
 - ② Maxima are spaced half-wavelength apart
 - ③ Minima are also spaced half-wavelength apart on Tx line.
 - ④ distance b/w maximum & minimum is quarter-wavelength

V & I distributions along oc lines :-

① In high frequency lossless line:
The values of the different maximum are equal as shown below.


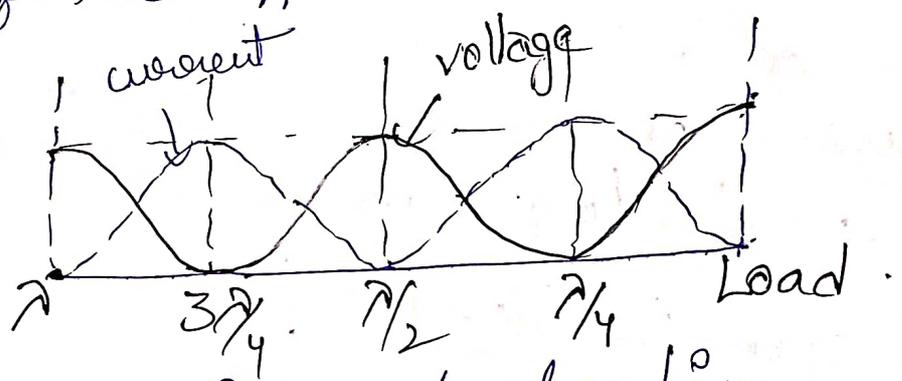


Fig (a) : Lossless line.

② In lossy line :-

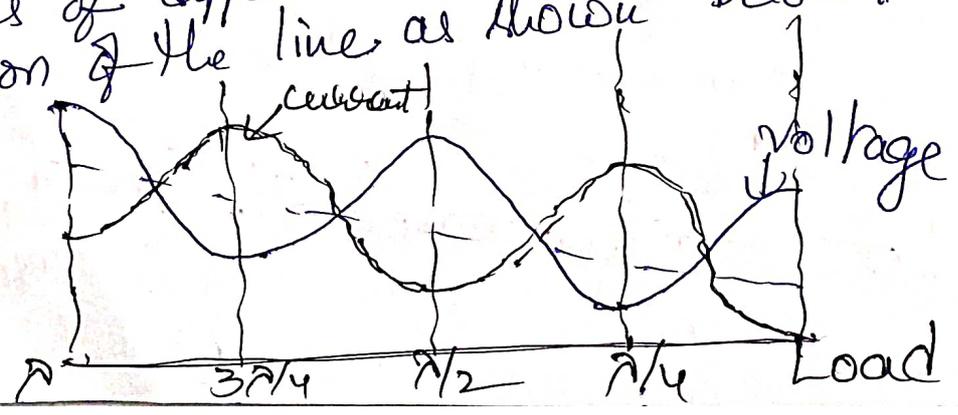The values of different maxima goes on decreasing due to attenuation of the line as shown below:



② Short-circuited Lines:

→ At short-circuited termination, current is maximum

& $V=0 \Rightarrow \boxed{Z=0}$

→ The standing waves thus has a node (or) minimum at the short-circuited end and at every $\lambda/2$ length from end


Note:- (i) V & I distributions differs from OC lines. i.e. (V & I are interchanged).

(ii) The voltage on the line goes through:
(i) Minima at distances from load at even multiples of $\lambda/4$.


(ii) Maxima that are odd multiples of $\lambda/4$.

→ Consider V & I distributions along SC lines are:

① Lossless line:

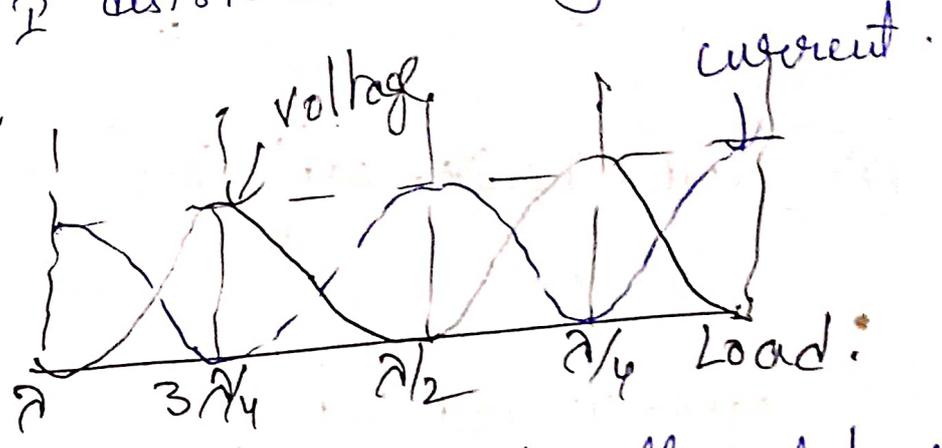

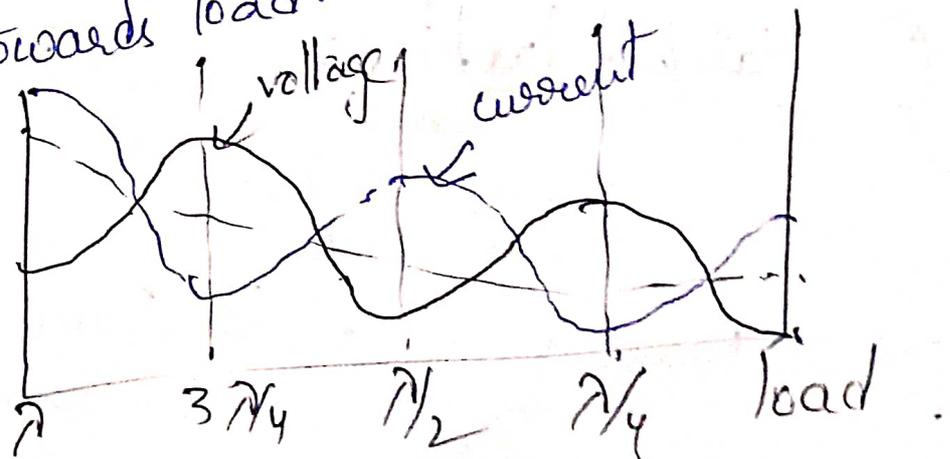② Lossy line: The voltage & current gets attenuated as they travel towards load.



Voltage standing wave ratio (VSWR)?

→ VSWR is the ratio of maximum voltage to minimum voltage of a standing wave.

voltage to

$$\boxed{VSWR (= \rho) = \frac{V_{\max}}{V_{\min}}}$$

also, $\boxed{CSWR = \frac{P_{\max}}{P_{\min}}}$

where $V_{\max} = |V_i| + |V_r| \rightarrow$ Maximum voltage when both waves add in phase.

$V_{\min} = |V_i| - |V_r| \rightarrow$ Minimum voltage when both waves add in opposite phase.

$$\therefore VSWR = \frac{|V_i| + |V_r|}{|V_i| - |V_r|} = \frac{1 + \left| \frac{V_r}{V_i} \right|}{1 - \left| \frac{V_r}{V_i} \right|} = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

$$\boxed{VSWR = \frac{1 + |\Gamma|}{1 - |\Gamma|}}$$

various load conditions:

① Short-circuited load: $\boxed{Z_R = 0}$ then $\Gamma_L = -1$

$$VSWR = \frac{1 + |\Gamma|}{1 - |\Gamma|} = \frac{1 + 1}{1 - 1} = \infty$$

② open-circuited load: $\boxed{Z_R = \infty}$ then $\Gamma_L = 1$

$$VSWR = \frac{1 + |\Gamma|}{1 - |\Gamma|} = \frac{1 + 1}{1 - 1} = \infty$$

③ Matched load: $\boxed{Z_R = Z_0}$ then $\Gamma_L = 0$

$$VSWR = \frac{1 + 0}{1 - 0} = 1$$

Note: Range of VSWR is from $\boxed{1 \text{ to } \infty}$

VHF lines as Circuit Elements (SC & OC Lines)

Different lengths of $\frac{(OS)}{Tx}$ Lines with SC & OC load:-

→ At high frequencies ($> 150 \text{ MHz}$), ordinary lumped circuit elements become difficult to construct. Thus Tx lines can be used as circuit elements as their size becomes very small.

→ A Tx lines operated at a frequency range from 300 MHz to 3 GHz are known as ultra-high frequency (UHF) lines.

→ At radio frequencies (RF) lines, UHF lines:-

$$\begin{array}{l} \omega L \gg R \\ \omega C \gg G \end{array}$$

characteristics of RF/UHF lines:-

→ From low-loss Tx lines (refer unit-1)

① propagation constant (P):-
attenuation constant $\alpha = \frac{1}{2} \left(R \sqrt{\frac{C}{L}} + G \sqrt{\frac{L}{C}} \right)$

Phase constant $\beta = \omega \sqrt{LC}$

Note:- G -neglected for air, dielectric lines.

② characteristic impedance (Z_0):-

$$Z_0 = \sqrt{\frac{L}{C}} \text{ — purely resistive}$$

(i) Under Short-circuited (SC) load:

Assume:- line to be lossless line.


$$\therefore Z_{SC} = jZ_0 \tan \beta l$$

$$= jZ_0 \tan \left(\frac{2\pi}{\lambda} \cdot l \right)$$

Note:- βl - electrical length.


Case (i): $0 < l < \lambda/4$; $l=0$; $\beta l = \frac{2\pi}{\lambda} \cdot 0 = 0^\circ$

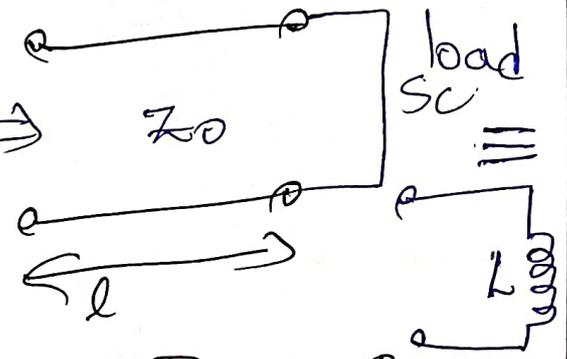$l = \lambda/4$; $\beta l = \frac{2\pi}{\lambda} \cdot \lambda/4 = \pi/2 = 90^\circ$



Thus, the short-circuited lines can provide inductive reactance of any value & length by selecting suitable length.

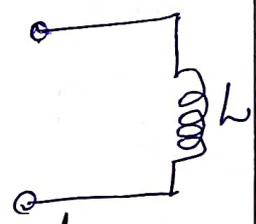\therefore The equivalent inductance impedance is obtained by equating, $j\omega L_{eq} = jZ_0 \tan \beta l$



$$\Rightarrow L_{eq} = \frac{Z_0}{\omega} \tan \beta l$$

it acts as an inductor.

Note:- \tan value $\rightarrow +ve$; $Z_{SC} \rightarrow$ inductive reactance.

Case (ii): $\lambda/4 < l < \lambda/2$; $l = \lambda/4$; $\beta l = \frac{2\pi}{\lambda} \cdot \lambda/4 = \pi/2 = 90^\circ$

$l = \lambda/2$; $\beta l = \frac{2\pi}{\lambda} \cdot \lambda/2 = \pi = 180^\circ$


$$-j \frac{1}{\omega C_{eq}} = j Z_0 \tan \beta l$$

$$C_{eq} = \frac{1}{\omega Z_0 \tan \beta l}$$

$\tan(90^\circ \text{ to } 180^\circ) \rightarrow -ve$ value

$\Rightarrow Z_{SC}$ is $-ve$.

\therefore It behaves as a capacitor.


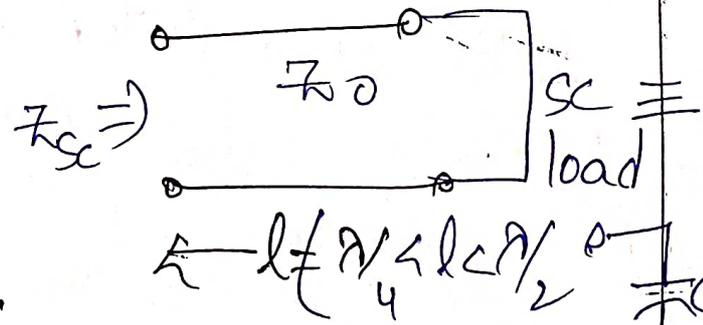


Case (iii): $l = \lambda/4$


It behaves as Quarter-wave transformer.

$Z_{in} = \frac{Z_0^2}{Z_R} = \infty$ (since $Z_R = 0$ for SC).

odd multiples of $\lambda/4$:

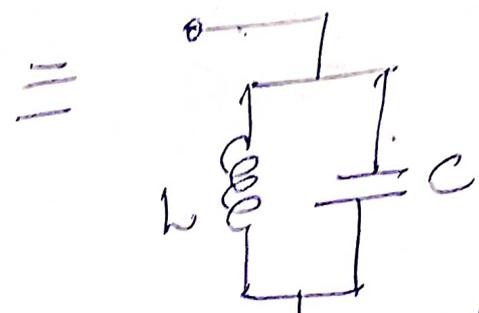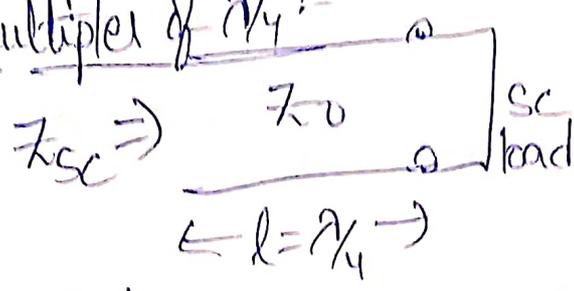


even multiples of $\lambda/4$:

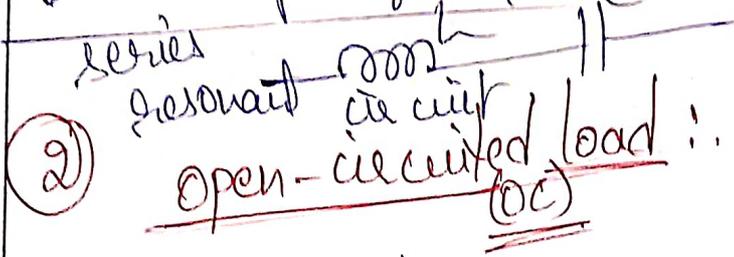

Parallel resonant circuit.

→ For lossless line:


$Z_{oc} = -j Z_0 \cot \beta l$

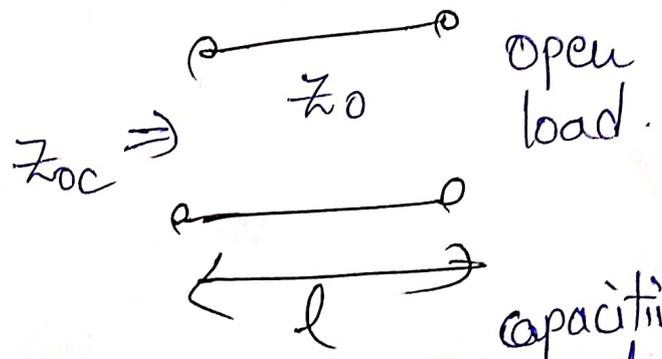

Case (i): $0 < l < \lambda/4$

→ Thus, the open-circuited lines can provide reactances of any value by selecting suitable length.

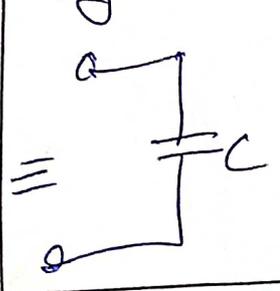∴ The equivalent capacitance impedance is given by $Z_{oc} = -j Z_0 \cot \beta l$ (angle 0 to 90, cot is +ve)



$\frac{1}{j \omega C_{eq}} = -j Z_0 \cot \beta l$

$C_{eq} = \frac{1}{\omega Z_0 \cot \beta l}$

$Z_{oc} \rightarrow$ -ve reactance
it acts as capacitor.


Case ②: $\frac{\lambda}{4} < l < \frac{\lambda}{2}$: Angle 90° to 180°
 cot is -ve


$$j\omega L_{eq} = -jZ_0 \cot \beta l$$

$L_{eq} = \frac{-Z_0 \cot \beta l}{\omega} \Rightarrow Z_{oc} \Rightarrow +ve$ reactance \rightarrow acts as inductor.

Case ③: $l = \frac{\lambda}{4}$: it is quarter wave transformer.

$$Z_{in} = \frac{Z_0^2}{Z_R} = 0 \quad (\text{since } Z_R = \infty \text{ for open load})$$

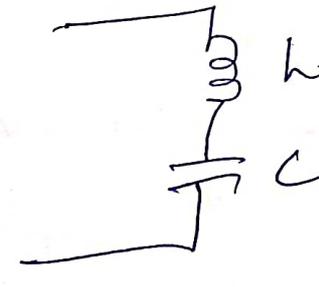odd multiples of $\frac{\lambda}{4}$ \equiv  series resonant circuit.

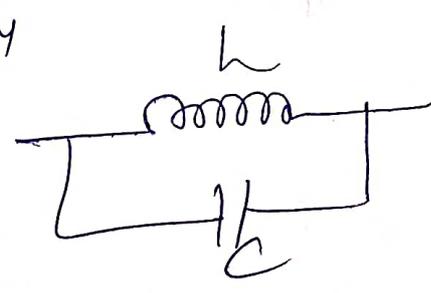even multiples of $\frac{\lambda}{4}$ \equiv  parallel resonant circuit.

Infinite length of Tx line:

$$Z_{in} = Z(l) = Z_0 \left[\frac{1 + \Gamma_L e^{-2\beta l}}{1 - \Gamma_L e^{-2\beta l}} \right]$$

$$Z(l = \infty) = Z_{in} = Z_0 \left[\frac{1 + \frac{\Gamma_L}{e^{2\beta l}}}{1 - \frac{\Gamma_L}{e^{2\beta l}}} \right]$$

$Z_{in} = Z_0 \Rightarrow Z_0 \left[\frac{1 + \frac{\Gamma_L}{e^{2\beta \infty}}}{1 - \frac{\Gamma_L}{e^{2\beta \infty}}} \right] = Z_0$ $(\frac{2\beta \infty}{e} = \infty)$

Impedance Matching Techniques:

→ When the Tx line is terminated with a load impedance which is not equal to characteristic impedance of the Tx line, mismatch occurs; thus reflections exist on the line.

- Mismatch — ① Reduces efficiency
② increases power loss

Remedy: -

To avoid mismatching, it is necessary to add impedance matching device between the load and the line.

- 2 techniques: - ① Quarter-wave transformer
② Stub Matching.

① Quarter-wave impedance matching (or) Quarter wave transformer:

→ when the Tx line is mismatched, a quarter wave line is inserted between the line and load to match load impedance to the line as shown in fig:

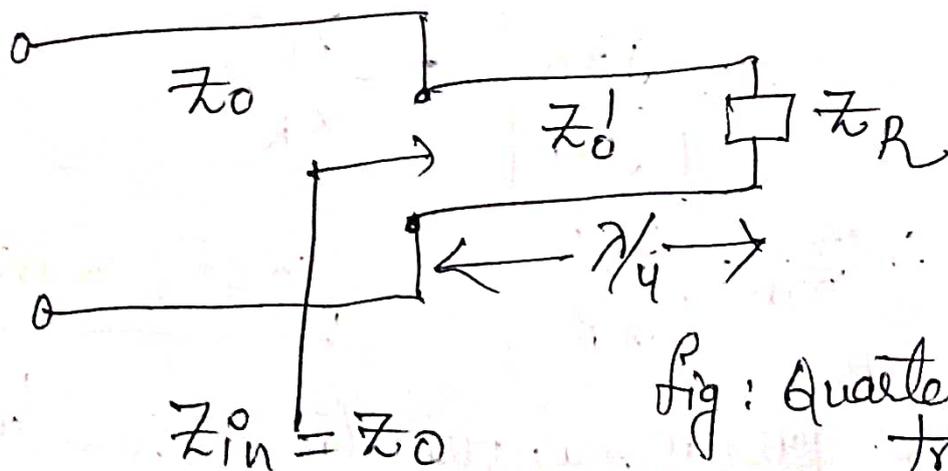


Fig: Quarter-wave transformer.

→ Z_0 is selected such that $Z_{in} = Z_0$

$$Z_0 = \sqrt{Z_0 Z_R}$$

∴ The quarter-wave transformer is also called $\lambda/4$ line.


Advantages: ① Simple to design.

Disadvantages: ① Need to cut the line to insert a quarter-wave transformer in between the line and the load.

② It is frequency sensitive.

Analysis: - $l = \lambda/4$
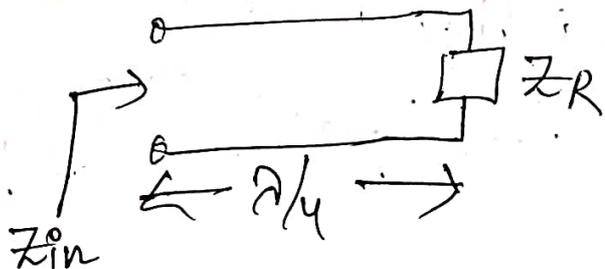
$$\beta l = \frac{2\pi}{\lambda} \times \lambda/4 = \pi/2$$



We know that:

$$Z_{in} = Z_0 \left[\frac{Z_R + j Z_0 \tan \pi/2}{Z_0 + j Z_R \tan \pi/2} \right] \quad \text{for lossless line}$$

$$= Z_0 \left[\frac{\frac{Z_R}{\tan \pi/2} + j Z_0}{\frac{Z_0}{\tan \pi/2} + j Z_R} \right] \quad (\text{since } \tan \pi/2 = \infty)$$

$$= Z_0 \left[\frac{j Z_0}{j Z_R} \right] = \frac{Z_0^2}{Z_R}$$

$$\therefore Z_{in} = \frac{Z_0^2}{Z_R}$$

$$Z_0 = \sqrt{Z_{in} Z_R}$$

Note! - As Z_R - purely real, use this for real loads but not for complex loads.

Steps for smith chart :- (Quarter wave transformer)

- ① Normalize the load impedance.

$$Z_R = 100 + j100 \Omega \quad Z_r = \frac{100 + j100}{50} = 2 + j2 \Omega$$

$$Z_0 = 50 \Omega$$

Point Z_r on smith chart & extend the line upto periphery (on periphery mark $l \approx 0.25 \lambda$).

- ② Draw constant VSWR circle.

Draw a circle from centre OZ_r as radius, draw a circle from centre O it will intersect, positive real axis at 4.2 .
 0.25λ i.e here, convert complex load impedance into real: $\text{char. value} = 4.2 \times 50 = 210 \Omega$.

- ③ Find Z_0' of $\lambda/4$ line:

$$Z_0' = \sqrt{Z_{in} Z_R} = \sqrt{50 \times 210} = 102.46 \Omega \approx 102 \Omega$$

- ④ Move point (4.2) to (2.04) on centre line.
(due to new Z_0')

$$\therefore \text{Normalized impedance} = \frac{210}{102} = 2.04 \approx 2$$

- ⑤ Draw constant VSWR circle and read the intersection point value after $\lambda/4$ length.

$$[0.49] \approx 0.5$$

- ⑥ Denormalize with char. imp of $\lambda/4$ line: $0.49 \times 102 = 50 \Omega$.


example 2:- $Z_L = 50 + j70 \Omega$

①

$$Z_0 = 50 \Omega$$

$$Z_L = 1 + j1.4$$

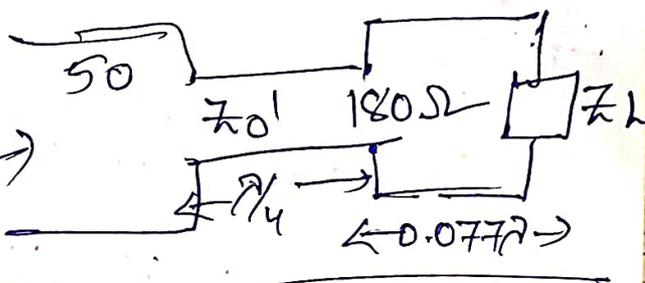Mark $l = 0.173 \lambda$. $Z_{in} = 50 \Omega$.



$$\begin{aligned} &0.25\lambda - 0.173\lambda \\ &0.077\lambda \end{aligned}$$

② real $Z_{in} = 3.6 @ 0.25\lambda$.

draw circle

$$\text{exact} = 3.6 \times 50 = 180 \Omega$$

value

③ $Z_0' = \sqrt{180 \times 50} = 95 \Omega$.

④ $\frac{180}{95} \approx 2$. — Mark it on chart.

⑤ draw another (new) circle from 0 to 2 point as radius.

move $\frac{1}{4}$ length. react point (0.53)

⑥ denormalize

$$0.53 \times 95 = 50.35 \Omega$$

Z

Single Stub Impedance Matching

Stub :- It is a short section of the line which is connected to the Tx line to reduce reflections along the line.

→ The stub should be positioned at input admittance to be $1 + jX$. (since stub is connected in parallel (shunt) to Tx line).

→ The length of short circuited stub should be such that susceptance of stub should be $-jX$.

So, Total admittance


$$\text{at } PP' : Y = Y_1 + Y_2 = 1 + jX - jX = 1$$

From fig:

where,

d_s - distance of the stub from load.

l_s - length of the stub.

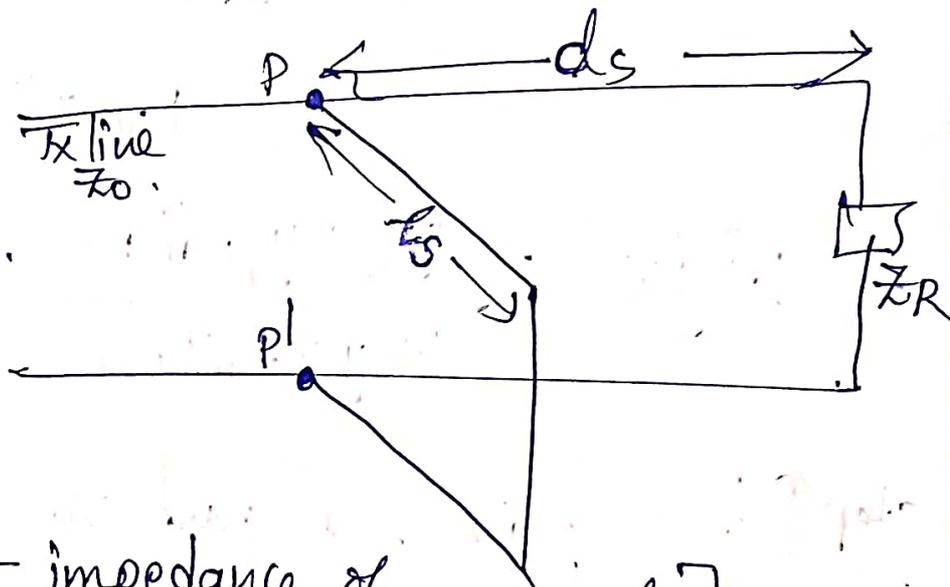

→ Consider, the input impedance of lossless Tx line

$$Z_{IN} = Z_0 \left[\frac{Z_R + jZ_0 \tan \beta l}{Z_0 + jZ_R \tan \beta l} \right]$$

Let $Z_{in} = \frac{Z_{IN}}{Z_0}$ → normalized input impedance

$Z_r = \frac{Z_R}{Z_0}$ → normalized load impedance.

$$\frac{z_{IN}}{z_0} = \frac{\frac{z_R}{z_0} + j \tan \beta l}{1 + j \frac{z_R}{z_0} \tan \beta l}$$

$$z_{in} = \frac{z_r + j \tan \beta l}{1 + j z_r \tan \beta l} \quad \text{--- Normalize w.r.t impedance}$$

Consider,
admittance $\frac{1}{y_{in}}$ = $\frac{\frac{1}{y_r} + j \tan \beta l}{1 + j \frac{1}{y_r} \tan \beta l}$ = $\frac{1 + j y_r \tan \beta l}{y_r + j \tan \beta l}$.
(since parallel stub)

$$\Rightarrow y_{in} = \frac{(y_r + j \tan \beta l)}{(1 + j y_r \tan \beta l)} \times \frac{(1 - j y_r \tan \beta l)}{(1 - j y_r \tan \beta l)}$$

$$= \frac{y_r - j y_r^2 \tan \beta l + j \tan \beta l + y_r \tan^2 \beta l}{1 + y_r^2 \tan^2 \beta l}$$

$$\Rightarrow 1 + jX = \frac{y_r + y_r \tan^2 \beta l}{1 + y_r^2 \tan^2 \beta l} + \frac{j(\tan \beta l - y_r^2 \tan \beta l)}{1 + y_r^2 \tan^2 \beta l}$$

Step 1:- To find location of stub:-
Equate real part to 1

$$\frac{y_r + y_r \tan^2 \beta l_s}{1 + y_r^2 \tan^2 \beta l_s} = 1$$

($l_s = d_s$
 d_s - location of stub).

$$y_r + y_r \tan^2 \beta l_s = 1 + y_r^2 \tan^2 \beta l_s$$

$$y_r \tan^2 \beta l_s (1 - y_r) = (1 - y_r)$$

$$Y_R \tan^2 \beta d_s = 1$$

$$\Rightarrow \tan^2 \beta d_s = \frac{1}{Y_R} = Z_R = \frac{Z_R}{Z_0}$$

$$\Rightarrow \tan \beta d_s = \sqrt{\frac{Z_R}{Z_0}}$$

$$\Rightarrow \beta d_s = \tan^{-1} \sqrt{\frac{Z_R}{Z_0}}$$

$$\Rightarrow \boxed{d_s = \frac{\lambda}{2\pi} \tan^{-1} \sqrt{\frac{Z_R}{Z_0}}} \rightarrow \text{location of stub expression.}$$

step 2: To find length of stub:-

→ Consider SC input impedance $Z_{sc} = jZ_0 \tan \beta l$
(since stub is short circuited at its end).

$$\frac{Z_{sc}}{Z_0} = j \tan \beta l = Z_{sc} \text{ — normalized SC input impedance.}$$

$$\therefore \frac{1}{Z_{sc}} = \frac{1}{j \tan \beta l} \Rightarrow \boxed{Y_{sc} = -j \cot \beta l}$$

Equate this admittance ^{of stub} to imaginary part of main Tx line

$$\cot \beta l_s = \frac{\tan \beta l_s - Y_R \tan \beta l_s}{1 + Y_R \tan \beta l_s}$$

$$\cot \beta l_s = \frac{\tan \beta l_s (1 - Y_R)}{1 + Y_R \tan \beta l_s}$$

$$\Rightarrow \cot \beta l_s = \frac{\sqrt{\frac{Z_R}{Z_0}} \left(1 - \frac{Z_0^2}{Z_R^2}\right)}{1 + \frac{Z_0}{Z_R} \times \frac{Z_R}{Z_0}} = \frac{Z_R \sqrt{\frac{Z_R}{Z_0}} \left(\frac{Z_R^2 - Z_0^2}{Z_R^2}\right)}{Z_R + Z_0}$$

$$\Rightarrow \cot \beta l_s = \frac{(\cancel{Z_R + Z_0})(Z_R - Z_0)}{\sqrt{Z_0 Z_R} (\cancel{Z_R + Z_0})}$$

since $\tan \beta l_s = \sqrt{\frac{Z_R}{Z_0}}$

$$Z_Y = \frac{Z_R}{Z_0}$$

$$Y_Y = \frac{1}{Z_Y} = \frac{Z_0}{Z_R}$$

$$\therefore \cot \beta l_s = \frac{Z_R - Z_0}{\sqrt{Z_R Z_0}}$$

$$\Rightarrow \tan \beta l_s = \frac{\sqrt{Z_R Z_0}}{Z_R - Z_0}$$

$$\Rightarrow \beta l_s = \tan^{-1} \left(\frac{\sqrt{Z_R Z_0}}{Z_R - Z_0} \right)$$

$$\Rightarrow l_s = \frac{\lambda}{2\pi} \tan^{-1} \left(\frac{\sqrt{Z_R Z_0}}{Z_R - Z_0} \right) \rightarrow \text{length of the stub.}$$


Note:-
Position of stub $l_s = \frac{\lambda}{2\pi} \left[\phi + \pi - \cos^{-1}(|\Gamma|) \right]$

length of stub $l_s = \frac{\lambda}{2\pi} \tan^{-1} \left(\frac{\sqrt{1 - |\Gamma|^2}}{2|\Gamma|} \right)$

in terms of reflection coefficient.

Single stub Matching using smith chart!

Given

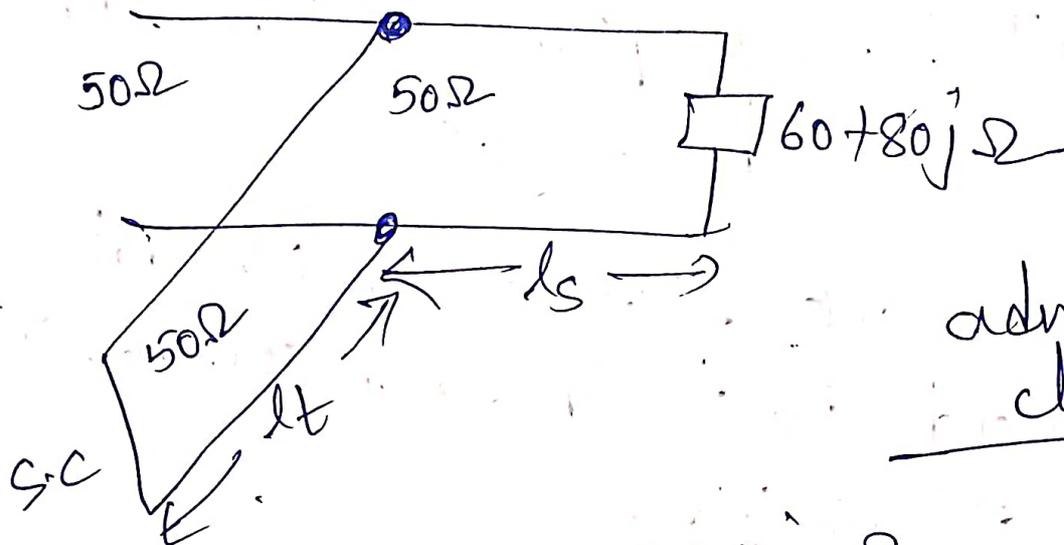

admittance chart


① Normalize load $Z_L = 60 + 80j\Omega$

$$Z_L = \frac{60 + 80j}{50} = 1.2 + 1.6j$$

Mark it on smith chart

② draw a line 0 to Z_L

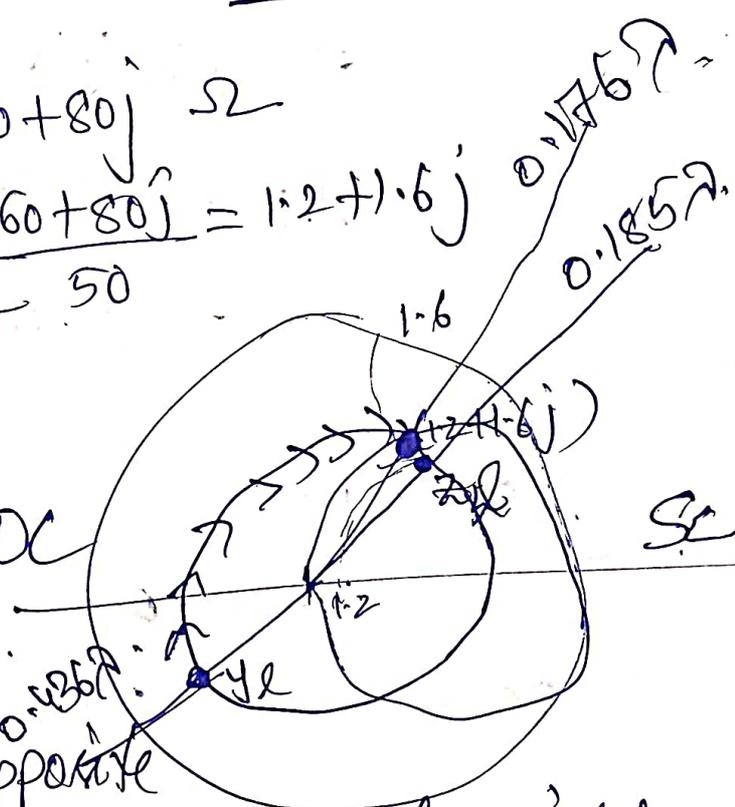③ Draw a VSWR circle OC from 0 to $(0.7Z_L)$ as radius.



Now extend $0Z_L$ line opposite direction which intersects VSWR circle gives load admittance (Y_L).

④ From load point (Y_L) move towards generator along the circle until it intersects unit circle.

$$l_s = 0.5\lambda - 0.436\lambda \quad l_s = 0.176 - 0.436\lambda = -0.260\lambda$$

$$= 0.064\lambda \text{ (or)}$$

$$= 0.064\lambda + 0.176\lambda = 0.240\lambda$$

$$= -0.260 + 0.5\lambda$$


$$= 0.240\lambda$$

Now we reached a point $1 + j1.5$
 To get 1, susceptance of the stub should be $-j1.5$.

Now mark $-j1.5$ on smith chart & extend line to it from center, cutting at 0.344λ .

$$l_t = 0.344\lambda - 0.25\lambda \\ = 0.094\lambda$$

Solution:-

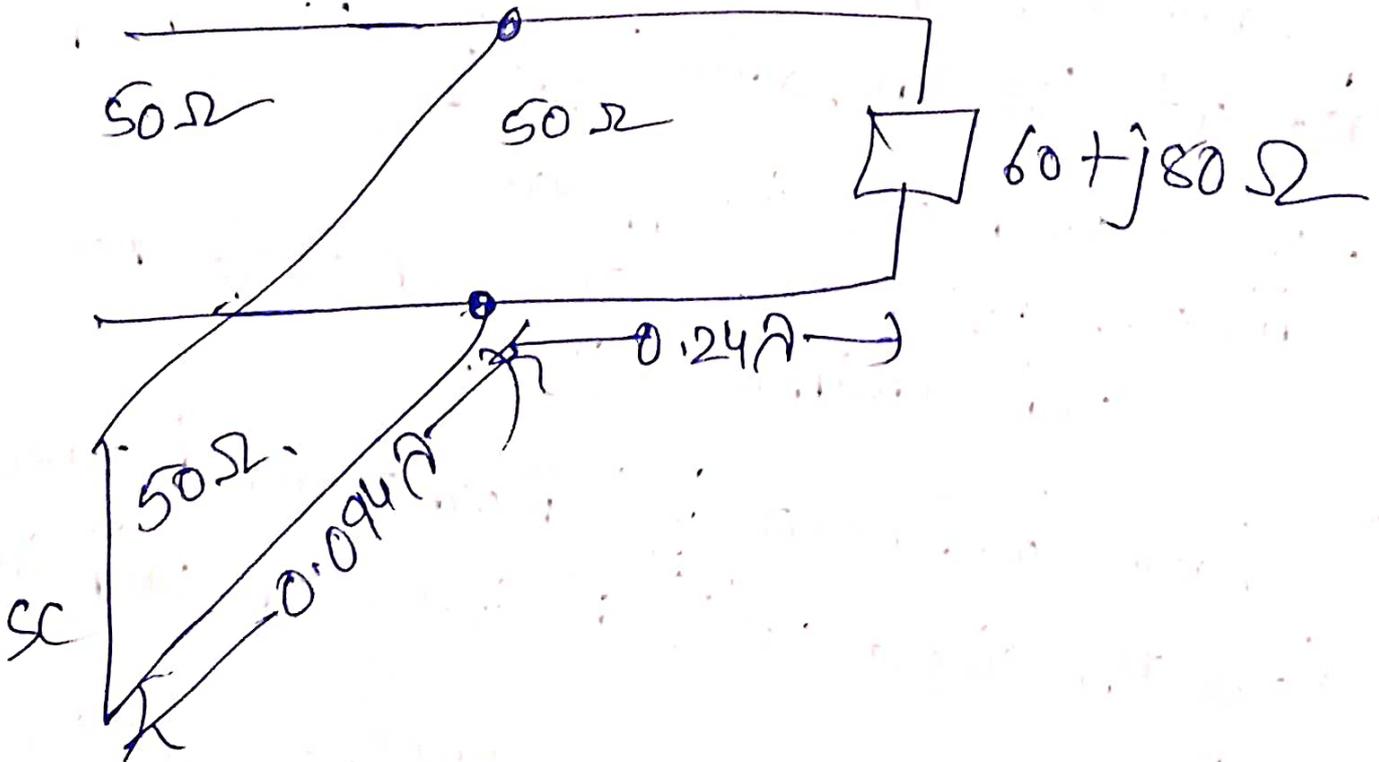

Z.

Smith chart

→ In 1939, Phillip Hagar Smith — an electrical engineer at bell telephone laboratories invented smith chart.


→ It is a graphical representation of reflection coefficient in complex plane. (or) It is a polar plot of γ & α -circles in the complex reflection coefficient plane.

Normalized

$$\text{impedance } (Z_r) = \frac{Z_R}{Z_0} = \frac{50 + j100}{100}$$

$$= 0.5 + j1$$

$$= \gamma + j\alpha$$

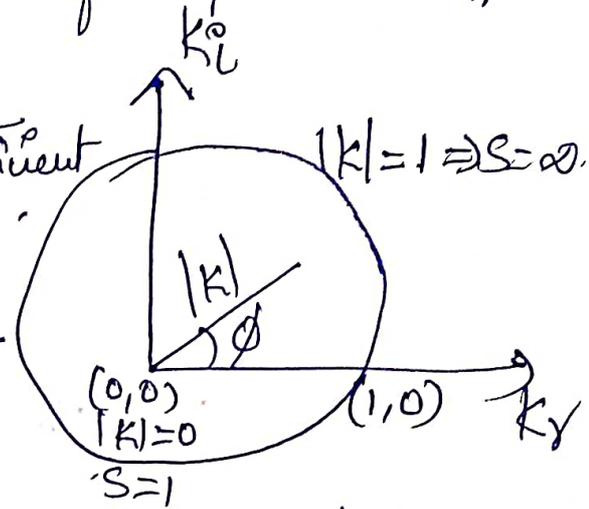

$$K = |K| \angle \phi$$

$$|K| \leq 1$$

∴ it consists 2 orthogonal circles

(i) γ -circles (resistance)

(ii) α -circles (reactance)

$$\text{Let } k_r = \frac{Z_R - Z_0}{Z_R + Z_0} = \frac{\frac{Z_R}{Z_0} - 1}{\frac{Z_R}{Z_0} + 1} = \frac{Z_r - 1}{Z_r + 1}$$

$$\Rightarrow Z_r = \frac{1 + k_r}{1 - k_r} \quad (\text{since } k \text{ is complex quantity})$$

$$\text{Let } k = k_r + j k_x$$

$$\therefore Z_r = \frac{1 + k_r + j k_x}{1 - k_r - j k_x}$$

— basis for construction of γ & α -circles.

Constant Resistance Circles:

$$Z_s = \frac{1+K}{1-K} = \frac{(1+k_r + jk_x)}{(1-k_r - jk_x)} \times \frac{(1-k_r + jk_x)}{(1-k_r + jk_x)}$$

$$= \frac{1 - k_r + jk_x + k_r - k_r^2 + jk_x k_r + jk_x - jk_x k_x - k_x^2}{(1-k_r)^2 + k_x^2}$$

$$\delta + j\alpha = \frac{1 - k_r^2 - k_x^2 + 2jk_x}{(1-k_r)^2 + k_x^2}$$

equating real parts & imaginary parts

$$\delta = \frac{1 - k_r^2 - k_x^2}{(1-k_r)^2 + k_x^2}$$

$$\alpha = \frac{2k_x}{(1-k_r)^2 + k_x^2}$$

Consider, δ -expression & multiply crossly

$$\delta \left[(1+k_r^2 - 2k_r) + k_x^2 \right] = 1 - k_r^2 - k_x^2$$

$$\delta + \delta k_r^2 - 2\delta k_r + \delta k_x^2 = 1 - k_r^2 - k_x^2$$

$$\delta + (\delta+1)k_r^2 + (\delta+1)k_x^2 - 2\delta k_r = 1$$

$$\Rightarrow (\delta+1)k_r^2 + (\delta+1)k_x^2 - 2\delta k_r = 1 - \delta$$

divide by $(\delta+1)$ term

$$k_r^2 + k_x^2 - \frac{2\delta}{\delta+1} k_r = \frac{1-\delta}{\delta+1}$$

$$\left(kx - \frac{x}{x+1}\right)^2 - \left(\frac{x}{x+1}\right)^2 + kx^2 = \frac{1-x}{x+1}$$

$$\left(kx - \frac{x}{x+1}\right)^2 + kx^2 = \frac{1-x}{x+1} + \frac{x^2}{(x+1)^2}$$

$$\leq \frac{1-x+x}{(x+1)^2} = \frac{1}{(x+1)^2}$$

$$\therefore \left(kx - \frac{x}{x+1}\right)^2 + kx^2 = \frac{1}{(x+1)^2}$$

This is equation of the circle of standard form

$$(x-h)^2 + (y-k)^2 = a^2$$

with centre (h, k)
& radius a


$$\text{Center} = \left(\frac{x}{x+1}, 0\right)$$

$$\text{Radius} = \frac{1}{x+1}$$

→ For different values of 'x' construct various circles:

x	Centre $\left(\frac{x}{x+1}, 0\right)$	Radius $\left(\frac{1}{x+1}\right)$
0	(0, 0)	1
0.5	(1/3, 0)	2/3
1	(1/2, 0)	1/2
2	(2/3, 0)	1/3
5	(5/6, 0)	1/6
∞	(1, 0)	0

point/dot

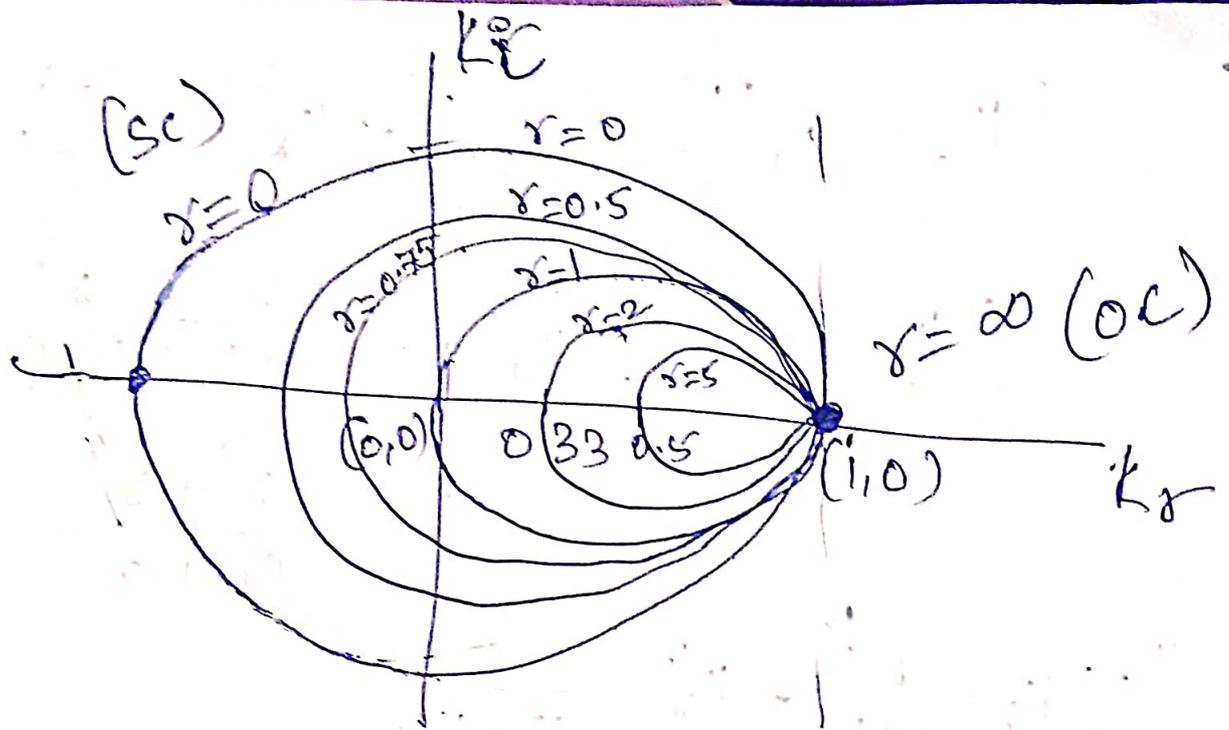

Constant Reactance Circles:

Take
$$x = \frac{2Kx}{(1-Kx)^2 + Kx^2}$$

$$(1-Kx)^2 + Kx^2 = \frac{2Kx}{x}$$

$$(1-Kx)^2 + Kx^2 - \frac{2Kx}{x} = 0$$

$$(1-Kx)^2 + \left(Kx - \frac{1}{x}\right)^2 - \frac{1}{x^2} = 0$$

$$(1-Kx)^2 + \left(Kx - \frac{1}{x}\right)^2 = \left(\frac{1}{x}\right)^2 \rightarrow \text{Equation of circle.}$$


$$\text{Center} = \left(1, \frac{1}{x}\right)$$

$$\text{radius} = \frac{1}{x}$$

Note: - 'x' may be either +ve (or) -ve.

→ For different values of x , various circles are?

x	centre $(1, \frac{1}{x})$	radius $(\frac{1}{x})$
0	$(1, \infty)$	∞
$\pm \frac{1}{2}$	$(1, \pm 2)$	2
± 1	$(1, \pm 1)$	1
± 2	$(1, \pm \frac{1}{2})$	$\frac{1}{2}$
± 5	$(1, \pm \frac{1}{5})$	$\frac{1}{5}$
$\pm \infty$	$(1, 0)$	0

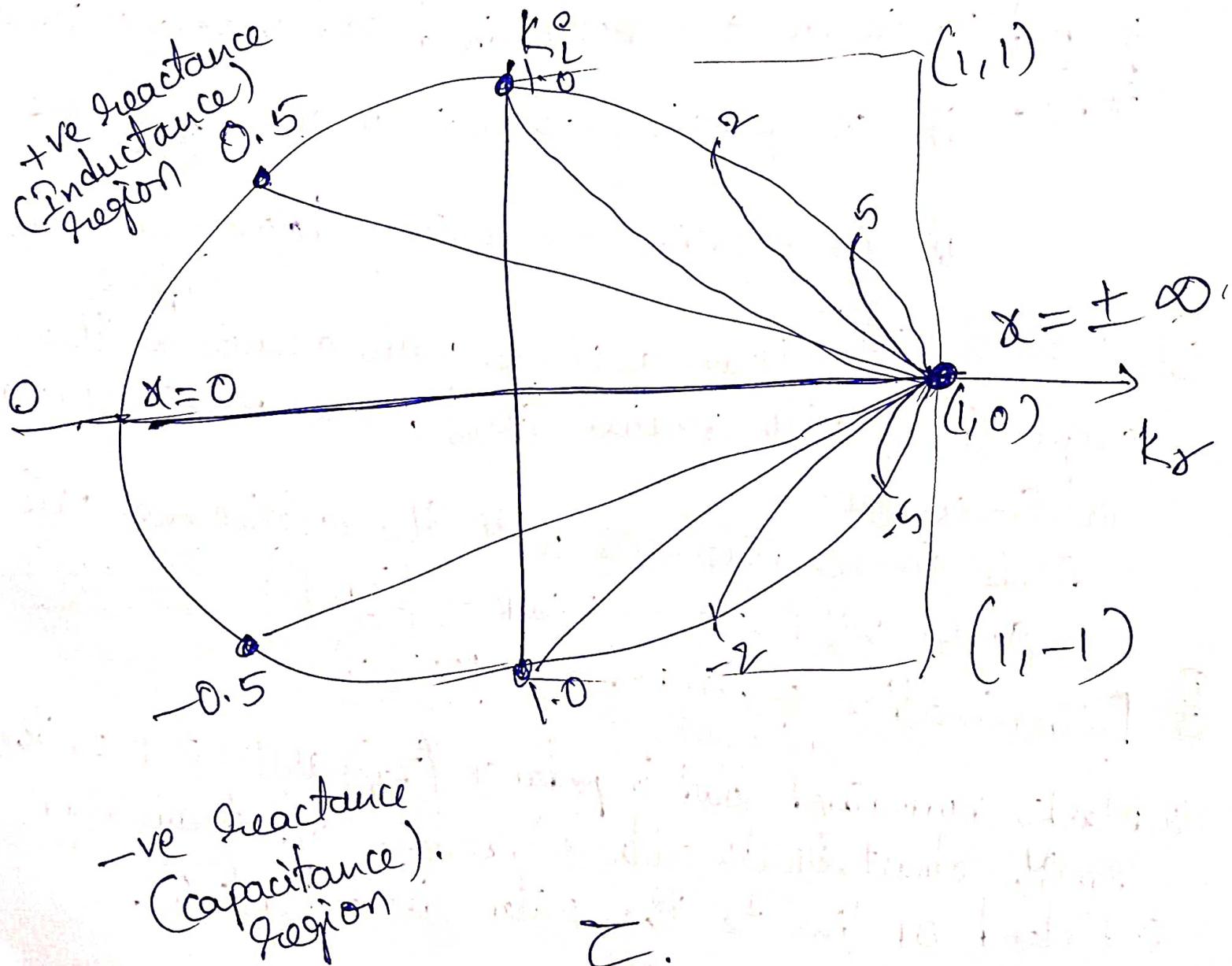

Properties of Smith chart:

① Normalisation of impedance: The Smith chart represents the normalised values of R and X circles.

$$\text{if } Z_R = R_R + jX_R \text{ — load impedance } \left. \vphantom{Z_R} \right\} \text{ of a lossless line}$$
$$Z_0 = \text{characteristic impedance}$$

then normalized values are $r = \frac{R_R}{Z_0}$ & $x = \frac{X_R}{Z_0}$

• Again, to obtain actual values, normalized values should be multiplied by Z_0 .

② Load Impedance plot: - The intersection points of R and X -circles give normalised load impedance values

(Z_R). if X -positive \rightarrow point is above real axis ($T_R = 0$).

if X -negative \rightarrow point is below real axis. ($T_R = 0$)

③ VSWR plot: - Draw a circle with a centre at the origin $(0, 0)$ with radius $|Z_R|$, called as VSWR circle or S -circles.

• This circle intersects with the positive real axis gives VSWR. ($VSWR = \left| \frac{Z_R}{Z_0} \right|$) $S = OM$

④ Determination of Z_{in} impedance point: -

① Mark normalised load impedance (Z_R) as point P on the Smith chart. ② With centre (0) , radius (OP) draw VSWR circle.

③ Extend OP line to the outer circle (Mark Q).

- ④ Rotate towards the generator (clockwise) upto a length $\lambda/2$. (Mark T)
- ⑤ Draw a line OT which cuts VSWR circle at point gives Z_{in} (normalised input impedance) (Mark N)
- ⑥ The angle NOP gives electric length (βl) of the line.
- ⑤ Determination of admittance point:-

$$\frac{Z_{in}}{Z_0} \times \frac{Z_R}{Z_0} = 1 \quad (\& \text{) } Z_{in} \times Z_R = 1$$

$$\Rightarrow \boxed{Y_R = Z_{in}} \quad \left(\text{since } Y_R = \frac{1}{Z_R} \right)$$

• After locating Z_{in} (impedance point), rotate it to a distance $\lambda/4$ (quarter wave) towards generator (clockwise).

\therefore As the $\lambda/4$ distance gives opposite point on chart, point opposite to impedance point on circle gives the admittance point.

- ⑥ Determination of the load impedance:-
- Consider a Tx line of length (l), Given VSWR & location of V_{min} from load. Then,

• To locate the load impedance:

- Draw S-circle with centre 'O' and radius VSWR.
- Locate point (A) on the outer circle at the left side end of the horizontal axis as position of V_{min} .
- Move towards the load (clockwise) to a given length l/λ on the wavelength scale and locate the point P'. Draw the line OP' which cuts S-circle at P.

→ The location of point P gives normalised load impedance

⑦ Input impedance & admittance of a SC (short-circuited) line:

→ Z_{in} of an SC line is purely reactive & $R = 0$.

→ The SC termination represents position of V_{min} i.e. point A on outer circle at left side end.

→ From point A, move towards generator (anti-clockwise) to a given length l/λ on wavelength scale & locate the point P, gives normalised input impedance of the SC line.

→ The opposite point Q gives the normalised input admittance.

⑧ Input impedance & admittance of an OC (open-circuited) line

→ Z_{in} of OC line is purely reactive & $R = \infty$.

→ The OC termination represents position of V_{max} i.e. point B on outer circle at right side end.

→ From point B, move towards generator to a given length l/λ on wavelength scale & locate point P.

→ P gives normalised input impedance of OC line

→ The opposite point Q gives normalised input admittance.

⑨ Determination of locations & lengths of stubs:

→ Impedance matching can be easily done by using Smith charts.

→ locations & lengths of stubs (single/double) can be obtained by locating the admittances on the chart.

→ Since the stubs are connected in parallel, it is much easier to combine admittance in parallel than impedances.

→ Also, SC stubs are preferred over OC stubs to avoid radiation losses;

≅

Applications of Smith Chart:-

① Smith chart as an admittance diagram:-

→ Generally, Smith chart is used as an impedance diagram, Z obtained from intersection of R & X circles.

→ Also, Smith chart is used for admittance:

• Normalised admittance $Y = G + jB$

where $G = \frac{1}{R}$ normalised conductance.

$B = \frac{1}{X}$ normalised susceptance.

$$\therefore \text{At termination, } Y_r = \frac{1}{Z_r} = \frac{1}{R + jX} = \frac{R - jX}{R^2 + X^2}$$

$$\therefore G - jB = \frac{R}{R^2 + X^2} - j \frac{X}{R^2 + X^2}$$

$$\cdot \text{ Also } Y_r = \frac{1}{Z_r} = \frac{1 - \Gamma}{1 + \Gamma}$$

$$\therefore G - jB = \frac{1 - \Gamma}{1 + \Gamma}$$

The G and B circles on T -plane can be drawn similar to R and X circles.

→ A Smith chart with G and B circles is called an admittance diagram.

∴ The admittance diagram is the mirror image of the impedance diagram; all measurements will be taken in reverse direction.

Converting impedance into admittance:

→ For a lossless quarter wave transformer, the input impedance is $Z_{in} = \frac{Z_0^2}{Z_R}$.

② Reflection coefficient values:

→ Draw the line OP & extend it to outer circle, cuts at Q.

∴ Magnitude of reflection coefficient is given by

$$|\Gamma| = \frac{OP}{OQ} \quad (\text{OP, OQ measure using scale})$$

$|\Gamma|$ can also be obtained from the Γ -scale provided in the chart.

→ The angles are indicated on the outer circle.
• The angle (ϕ) of the line OP (w.r.t +ve real axis) gives angle of reflection coefficient.

③ Location of V_{max} & V_{min} :

There are 2 intersection point of VSWR circle with the horizontal axis/real axis AB.

V_{\min} → The point at the left side of the centre represents voltage minima (V_{\min}). (Point L)

V_{\max} → The point at right side of the centre represents voltage maxima (V_{\max}) (Point M).

→ whereas, the locations can be obtained from wavelength scale on outer circle.

arc AQ → gives distance of V_{\min} from the load.

arc QAB → gives distance of 1st V_{\max} from load.

④ Open & short-circuited lines:-

→ At point 'B' on right side end of horizontal axis,
both $R = X = \infty \Rightarrow$ OC line.

→ At point 'A' on left side end of horizontal axis,
both $R = X = 0 \Rightarrow$ SC line.

Z .

UNIT II

Problems :

Transmission Lines - II

Given that

Open-circuited impedance, $Z_{oc} = 750 \Omega$.

Short-circuited impedance, $Z_{sc} = 500 \Omega$.

The characteristic impedance of a line is given by

$$Z_0 = \sqrt{Z_{oc} \times Z_{sc}} = \sqrt{750 \times 500} = \sqrt{375000}.$$

The characteristic impedance is $Z_0 = 612.37 \Omega$.

Find Characteristic Impedance (Z_0):

Example 10.13 $Z_{oc} = 900 \angle -30^\circ \Omega$, $Z_{sc} = 400 \angle -10^\circ \Omega$. Calculate the Z_0 and γ of a 12 km long line.

Solution Given: $Z_{oc} = 900 \angle -30^\circ \Omega$, $Z_{sc} = 400 \angle -10^\circ \Omega$.

a) The characteristic impedance is given by

$$Z_0 = \sqrt{Z_{oc} \times Z_{sc}} = \sqrt{900 \angle -30 \times 400 \angle -10} = 600 \angle -20^\circ \Omega.$$

Hence, the characteristic impedance, $Z_0 = 600 \angle -20^\circ \Omega$.

We know that $\tanh \gamma l = \sqrt{\frac{Z_{sc}}{Z_{oc}}}$.

$$\tanh \gamma l = \sqrt{\frac{400 \angle -10}{900 \angle -30}} = 0.67 \angle 10.$$

$$\frac{e^{\gamma l} - e^{-\gamma l}}{e^{\gamma l} + e^{-\gamma l}} = 0.66 - j0.116.$$

By componendo and dividendo principle,

$$\frac{2e^{\gamma l}}{2e^{-\gamma l}} = \frac{1 + 0.66 - j0.116}{1 - (0.66 - j0.116)}$$

$$e^{2\gamma l} = 4.269 - j1.798 = 4.632 \angle -22.8.$$

Taking ln of both sides,

$$2\gamma l = \ln(4.632 \angle -22.8^\circ).$$

$$\gamma = \frac{1}{2l} (\ln(4.632) + j(-22.8^\circ))$$

or $\gamma = \frac{1}{2 \times 12} (1.533 - j0.398).$

$$\gamma = \alpha + j\beta = 0.0638 - j0.01658 \text{ napers/km.}$$

Example 10.14 A two wire line has a characteristic impedance of 300Ω and is fed to a 90Ω resistor at 200 MHz. A quarter wave line is used as a tube 0.25 cm in diameter. Find the centre-to-centre spacing in air.

Componendo & dividendo rule:

If $\frac{a}{b} = \frac{c}{d}$ then

$$\frac{a+b}{a-b} = \frac{c+d}{c-d}.$$

Electromagnetic Waves and Transmission Lines

Solution Given: $Z_1 = 300 \Omega$, $Z_2 = 90 \Omega$, tube diameter = 0.25 cm, radius $r = 0.125$ cm.

For a quarter wave line, we know that

$$Z_0 = \sqrt{Z_1 \times Z_2} = \sqrt{300 \times 90} = 164.32 \Omega.$$

Also, we know that the characteristic impedance of a parallel wire line is,

$$Z_0 = 276 \log (d/r) \text{ ohms,}$$

where d = centre-to-centre spacing.

$$\therefore 164.32 = 276 \log \left[\frac{d}{0.125} \right].$$

$$\log \left[\frac{d}{0.125} \right] = 0.595.$$

$$\frac{d}{0.125} = 3.936 \text{ or } d = 0.49 \text{ cm.}$$

Example 10.15 A 60 ohm lossless line is connected to a source with 10 V, $Z_g = 50 - j40$ and terminated with a load of $j40$ ohms. If the line is 100 m long and $\beta = 0.25$ rad/m, calculate Z_{in} and voltage at (i) the sending end, (ii) the receiving end, (iii) 4 m from the load end and (iv) 3 m from the source.

Solution Given:

Length, $l = 100$ m, characteristic impedance, $Z_0 = 60$ ohms, termination impedance, $Z_R = j40$ ohms, source resistance, $Z_g = 50 - j40$ ohms, source voltage, $V_g = 10$ V, $\alpha = 0$, $\beta = 0.25$ rad/m;

$$\text{input current is } I_s = \frac{V_g}{Z_0 + Z_g} = \frac{10}{60 + 50 - j40} = 85.4 \angle 20 \text{ mA.}$$

We know that the source impedance for a lossless transmission line is

$$Z_s = Z_0 \left(\frac{Z_R + jZ_0 \tan \beta l}{Z_0 + jZ_R \tan \beta l} \right).$$

(i) At the sending end, $l = 100$ m, $\beta l = 0.25 \times 100 = 25 \text{ rad} = 1432.4^\circ$.

$$Z_s = 60 \left(\frac{j40 + j60 \tan 1432.4}{60 + j^2 40 \tan 1432.4} \right) = j29.38 \Omega.$$

$$\text{Input voltage is } V_s = Z_s I_s = j29.38 \times (85.4 \angle 20) \times 10^{-3} = 2.5 \angle 110 \text{ V.}$$

(ii) At the receiving end, $l = 0$.

$$Z_s = Z_R = j40 \Omega.$$

$$V_R = Z_R I_s = j40 \times (85.4 \angle 20) \times 10^{-3} = 3.416 \angle 110 \text{ V.}$$

(iii) At 4 m from the load end: $l = 4$, $\beta l = 0.25 \times 4 = 1 \text{ rad} = 57.3^\circ$.

$$Z_1 = 60 \left(\frac{j40 + j60 \tan 57.3}{60 + j^2 40 \tan 57.3} \right) = -j435.53 \Omega.$$

$$V_1 = Z_1 I_s = -j435.53 \times 85.4 \angle 20 \times 10^{-3} = 37.2 \angle -70^\circ \text{ V.}$$

(iv) At 3 m from the source end: $l = 97$, $\beta l = 0.25 \times 97 = 2425 \text{ rad} = 1389.4^\circ$.

$$Z_2 = 60 \left(\frac{j40 + j60 \tan 1389.4}{60 + j^2 40 \tan 1389.4} \right) = -j0.303 \Omega.$$

$$V_2 = Z_2 I_s = -j0.303 \times (85.4 \angle 20) \times 10^{-3} = 0.0258 \angle -70^\circ \text{ V.}$$

Example 10.16 An open wire unloaded line, 75 km long, is operated at a frequency of 1000 Hz. The open circuit impedance is found to be $330 \angle -30^\circ \Omega$ and the short circuit impedance is $540 \angle 7^\circ \Omega$. Calculate the parameters of line.

Solution Given: Length of the unloaded line, $l = 75 \text{ km}$, $f = 1000 \text{ Hz}$, $Z_{oc} = 330 \angle -30^\circ \Omega$, $Z_{sc} = 540 \angle 7^\circ \Omega$.

We know that $Z_0 = Z_{sc} \times Z_{oc}$

$$= \sqrt{540 \angle 7^\circ \times 330 \angle -30^\circ} = 422.14 \angle -11.5.$$

Also, $Z_{sc} = Z_0 \tanh \gamma l$.

$$\tanh \gamma l = \frac{Z_{sc}}{Z_0} = \frac{540 \angle 7^\circ}{422.14 \angle -23^\circ}$$

$$= 1.28 \angle 30^\circ = 1.108 + j0.64.$$

$$\frac{e^{\gamma l} - e^{-\gamma l}}{e^{\gamma l} + e^{-\gamma l}} = 1.108 + j0.64.$$

By componendo and dividendo principle,

$$\frac{2e^{\gamma l}}{2e^{-\gamma l}} = \frac{1 + 1.108 - j0.64}{1 - 1.108 - j0.64}$$

$$e^{2\gamma l} = \frac{2.108 + j0.64}{-0.108 - j0.64}$$

$$e^{2\gamma l} = \frac{2.203 \angle 16.89^\circ}{0.649 \angle -99.58^\circ} = 3.394 \angle 116.47^\circ.$$

Taking ln of both sides,

$$2\gamma l = \ln(3.394 \angle 116.47^\circ).$$

Since, $\ln(r \angle \theta) = \ln r + j\theta^\circ$,

$$\begin{aligned} \gamma &= \frac{1}{2l} (\ln(3.394) + j(116.47^\circ)) \\ &= \frac{1}{2l} (1.222 + j2.033) = \frac{1.222 + j2.033}{150} = 0.00815 + j0.0135. \end{aligned}$$

$$\gamma = 0.0157 \angle 58.88^\circ.$$

$$\beta = 0.00815 \text{ rad/km and } \alpha = 0.0135 \text{ nepers/km.}$$

Also we know that $= R + j\omega L$.

$$R + j\omega L = 0.0157 \angle 58.88^\circ \times 422.14 \angle -10.5^\circ = 6.627 \angle 47.38^\circ$$

$$R + j\omega L = 4.487 + j4.877.$$

$$R = 4.487 \Omega/\text{km and } \omega L = 4.877.$$

$$2\pi f \times L = 4.877.$$

$$L = \frac{4.877}{2\pi f} = \frac{4.877}{2 \times \pi \times 1000} = 0.776 \text{ mH/km.}$$

$$\frac{\gamma}{Z_0} = G + j\omega C.$$

$$G + j\omega C = \frac{0.0157 \angle 58.88^\circ}{422.14 \angle -10.5^\circ} = 3.72 \times 10^{-5} \angle 70.38^\circ$$

$$G + j\omega C = 12.5 \times 10^{-6} + j35 \times 10^{-6}.$$

$$G = 12.5 \mu\text{S}/\text{km and } \omega C = 3.5 \times 10^{-5}.$$

$$2\pi f C = 3.5 \times 10^{-5}.$$

$$C = \frac{3.5 \times 10^{-5}}{2\pi f} = \frac{3.5 \times 10^{-5}}{2 \times \pi \times 1000}$$

$$C = 5.576 \text{ nF/km.}$$

Example 10.17 The input impedance of a short circuited lossy transmission line of length 2 m and characteristic impedance 75Ω is $45 + j225 \Omega$.

(a) Find α and β of a line.

(b) Determine the input impedance if the short circuit is replaced by a load impedance of $67.5 - j45 \Omega$.

Solution Given: Input impedance of a short circuited line, $Z_{sc} = 45 + j225 \Omega$, characteristic impedance, $Z_0 = 75 \Omega$, length $l = 2$ m.

(a) We know that $Z_{sc} = Z_0 \tanh \gamma l$.

$$\tanh \gamma l = \frac{Z_{sc}}{Z_0} = \frac{45 + j225}{75} = 0.6 + j3.$$

$$\frac{e^{\gamma l} - e^{-\gamma l}}{e^{\gamma l} + e^{-\gamma l}} = 0.6 + j3.$$

By componendo and dividendo principle,

$$\frac{2e^{\gamma l}}{2e^{-\gamma l}} = \frac{1 + 0.6 - j3}{1 - 0.6 - j3}$$

$$e^{2\gamma l} = \frac{1.6 + j3}{0.4 - j3} = 1.12 \angle 114.3.$$

Taking ln of both sides,

$$2\gamma l = \ln(1.12 \angle 144.3^\circ).$$

Since, $\ln(r \angle \theta) = \ln r + j\theta^\circ$,

$$\gamma = \frac{1}{2l} (\ln(1.12) + j(144.3^\circ)) = \frac{0.1133 + j2.518}{2 \times 2} = 0.028 + j0.63.$$

$$\gamma = 0.0157 \angle 58.88^\circ; \beta = 0.63 \text{ rad/km and } \alpha = 0.028 \text{ nepers/km.}$$

(b) Given: Load impedance $Z_R = 67.5 - j45 \Omega$.

We know that the input impedance is

$$Z_{in} = Z_0 \left(\frac{1 + Ke^{-2\gamma l}}{1 - Ke^{-2\gamma l}} \right),$$

$$\text{where } K = \frac{Z_R - Z_0}{Z_R + Z_0} = \frac{67.5 - j45 - 75}{67.5 - j45 + 75} = 0.3 \angle -82^\circ.$$

$$e^{2\gamma l} = 1.12 \angle 114.3.$$

$$Z_{in} = 75 \left(\frac{1 + \frac{0.3 \angle -82}{1.12 \angle 144.3}}{1 - \frac{0.3 \angle -82}{1.12 \angle 144.3}} \right) = 75 \left(\frac{1 + 0.2678 \angle 226.3}{1 - 0.2678 \angle 226.3} \right) = 52.35 \angle 22.66.$$

Input impedance is $Z_{in} = 48.3 + j20 \Omega$.

Example 10.18 A dipole antenna is fed by a lossless transmission line having $Z_0 = 60 \Omega$. The source impedance is 600Ω . If the length of the line is 0.1λ , determine antenna impedance.

Solution Given: Length of the line $l = 0.1\lambda$, characteristic impedance, $Z_0 = 60 \Omega$, source impedance $Z_S = 600 \Omega$.

Let Z_R be the antenna impedance. We know that the source impedance for a lossless transmission line is

$$Z_S = Z_0 \left(\frac{Z_R + jZ_0 \tan \beta l}{Z_0 + jZ_R \tan \beta l} \right),$$

or $Z_R = Z_0 \left(\frac{Z_S - jZ_0 \tan \beta l}{Z_0 - jZ_S \tan \beta l} \right).$

Now $\tan \beta l = \tan \left[\frac{2\pi}{\lambda} (0.1\lambda) \right] = \tan (0.2\pi) = 0.726.$

$$\begin{aligned} \therefore Z_R &= 60 \left[\frac{600 - j60(0.726)}{60 - j600(0.726)} \right] = 60 \left[\frac{600 - j43.56}{60 - j435.6} \right] \\ &= 17.06 + j80.3 = 82.09 \angle 78^\circ. \end{aligned}$$

\therefore Antenna impedance is $Z_R = 82.09 \angle 78^\circ$.

Example 10.19 A transmission line of 100Ω characteristic impedance is connected to a load of 400Ω . Calculate the reflection coefficient and standing wave ratio.

Solution Given: Characteristic impedance, $Z_0 = 100 \Omega$, load, $Z_R = 400 \Omega$.

We know that reflection coefficient K is given by

$$K = \frac{Z_R - Z_0}{Z_R + Z_0} = \frac{400 - 100}{400 + 100}.$$

\therefore Reflection coefficient, $K = 3/5 = 0.6$.

The standing wave ratio is $VSWR = \frac{1 + |K|}{1 - |K|} = \frac{1 + 0.6}{1 - 0.6} = \frac{1.6}{0.4} = 4.$

Example 10.20 An UHF transmission line of $Z_0 = 150$ ohms is terminated with an unknown load. The VSWR measured in the line is 5 and the position of minimum current nearest the load is one-fifth wavelength away. Calculate the value of the load impedance.

Solution Given: Characteristic impedance, $Z_0 = 150$, $VSWR = S = 5$, position of minimum current $y_{\max} = \lambda/5$.

Position of the first minimum current or voltage maximum can be obtained by

$$2\beta y_{\max} - \phi = 0.$$

$$2 \cdot \frac{2\pi}{\lambda} \cdot \frac{\lambda}{5} - \phi = 0,$$

$$\text{or } \phi = \frac{4\pi}{5} = 2.51 \text{ radians or } 144^\circ.$$

We know that the magnitude of the reflection coefficient is

$$|K| = \frac{S-1}{S+1} = \frac{5-1}{5+1} = 0.666.$$

The reflection coefficient K is

$$K = |K|e^{j\phi} = 0.667 \angle 144^\circ.$$

$$\text{Also we know that } K = \frac{Z_R - Z_0}{Z_R + Z_0}.$$

$$0.667 \angle 144^\circ = \frac{Z_R - 150}{Z_R + 150}$$

$$-0.5388 + j0.3916 = \frac{Z_R - 150}{Z_R + 150}$$

$$Z_R(-0.5388 + j0.3916 - 1) = (-150 + 150 \times 0.5388 - j150 \times 0.3916)$$

$$Z_R(-1.5388 + j0.3916) = -69.18 - j58.74$$

$$Z_R = \frac{90.753 \angle -139.66^\circ}{1.588 \angle 165.72^\circ}$$

The load impedance, $Z_R = 57.15 \angle -305.38$ or $Z_R = 57.15 \angle 54.62 \Omega$.

Example 10.21 An open wire transmission line having $Z_0 = 650 \angle -12^\circ \Omega$ is terminated in Z_0 at the receiving end. If this line is supplied from a source of internal resistance 300Ω , calculate the reflection factor and reflection loss at the sending end terminals.

Solution Given: $Z_i = 300 \Omega$, $Z_0 = 650 \angle -12^\circ \Omega$.

We know that the reflection factor is

$$K_f = \frac{2\sqrt{Z_i Z_0}}{Z_i + Z_0}.$$

$$\therefore K_f = \frac{2\sqrt{300 \times 650 \angle -12^\circ}}{(300 + 6358 - j135)} = \frac{883 \angle -6^\circ}{945.5 \angle -8.22^\circ} = 0.934 \angle 2.22^\circ.$$

The reflection loss,

$$K_e = 20 \log_{10} \left| \frac{1}{K_f} \right| = 20 \log \left(\frac{1}{0.934} \right).$$

$$K_e = 0.59 \text{ dB.}$$

\therefore The reflection loss is 0.59 dB.

Example 10.22 A 80Ω distortionless line connects a signal of 50 kHz to a load of 140Ω . The load power is 75 mW . Calculate:

- (i) Voltage reflection coefficient,
- (ii) VSWR,
- (iii) Position of V_{\max} , I_{\max} , V_{\min} and I_{\min} .

Solution Given: $Z_R = 140 \Omega$, $Z_0 = 80 \Omega$.

- (i) Voltage reflection coefficient

$$K = \frac{Z_R - Z_0}{Z_R + Z_0} = \frac{140 - 80}{140 + 80} = 0.273.$$

$$\therefore K = 0.273, \phi = 0.$$

- (ii) VSWR

$$\text{VSWR} = \frac{1 + |K|}{1 - |K|} = \frac{1 + 0.273}{1 - 0.273} = 1.75.$$

- (iii) Position of V_{\max} , I_{\max} , V_{\min} and I_{\min}

The condition for maximum voltage occurs at y_{\max} from the load, i.e.,

$$2\beta y_{\max} - \phi = 2n\pi.$$

For first maximum, $n = 0$,

$$2\beta y_{\max} - \phi = 0$$

$$2\beta y_{\max} - 0 = 0, \quad y_{\max} = 0.$$

Therefore, the first voltage maximum, V_{\max} , and current minimum, I_{\min} , occur at the load position.

The first voltage minimum, V_{\min} , occurs at a distance of $\lambda/4$ from V_{\max} .

$$\therefore y_{\min} = y_{\max} + \lambda/4 = 0 + \lambda/4 = \lambda/4.$$

We know that the wavelength, $\lambda = \frac{v_0}{f} = \frac{3 \times 10^8}{50 \times 10^3} = 6 \text{ km}$.

$$\therefore y_{\min} = \frac{v_0}{4 \times f} = \frac{3 \times 10^8}{4 \times 50 \times 10^3} = 1.5 \text{ km}.$$

Therefore, the first voltage minimum and current maximum, I_{\max} occur at a distance of 1.5 km from the load. These values repeat every $\frac{\lambda}{2} = 3 \text{ km}$ distance from the load.

Given: The power at the load is $P = 75 \text{ mW}$.

We know that $P = \frac{V_{\max}^2}{Z_R}$ and $I_{\min} = \frac{V_{\max}}{Z_R}$.

V_{\max} at the load is $\sqrt{P \times Z_R} = \sqrt{75 \times 10^{-3} \times 140} = 3.24$ volts and $I_{\min} = \frac{3.24}{140} = 0.23$ mA.

Example 10.23 Design a quarter wave transformer to match a line having impedance of 300Ω to a load of 600Ω .

Solution Given: $Z_0 = 300 \Omega$, $Z_L = 600 \Omega$.

The quarter wave transformer should have a sending end impedance of

$$Z_S = \frac{Z_0^2}{Z_L} = \frac{300 \times 300}{600} = 150 \Omega.$$

The impedance will be matched if the Z_S of a $\lambda/4$ transformer is 150Ω .

Example 10.24 Calculate the reflection coefficient and VSWR of a 50Ω line terminated with (i) matched load, (ii) short circuit, (iii) $+j50 \Omega$ load, (iv) $-j50 \Omega$ load.

Solution

(i) Matched load

$$Z_0 = 50 \Omega, Z_R = 50 \Omega.$$

$$\text{Reflection coefficient } K = \frac{Z_R - Z_0}{Z_R + Z_0} = \frac{50 - 50}{50 + 50} = 0$$

$$\text{and VSWR } S = \frac{1 + |K|}{1 - |K|} = \frac{1 + 0}{1 - 0}.$$

$$\therefore S = 1$$

(ii) Short circuit

$$Z_R = 0, Z_0 = 50 \Omega.$$

$$K = \frac{Z_R - Z_0}{Z_R + Z_0} = \frac{0 - 50}{0 + 50} = -1.$$

$$S = \frac{1 + |K|}{1 - |K|} = \frac{1}{0} = \infty.$$

(iii) $+j50 \Omega$ load

$$\therefore Z_R = +j50 \Omega, Z_0 = 50 \Omega.$$

$$K = \frac{+j50 - 50}{j50 + 50} = \frac{-1 + j}{1 + j} = \frac{1.414 \angle 135^\circ}{1.414 \angle 45^\circ}$$

$$\therefore K = 1 \angle 90^\circ.$$

$$S = \frac{1 + |K|}{1 - |K|} = \frac{1 + 1}{1 - 1} = \frac{2}{0} = \infty.$$

(iv) $-j50 \Omega$ load

$$\therefore Z_R = -j50 \Omega, Z_0 = 50 \Omega.$$

$$K = \frac{-j50 - 50}{j50 + 50} = \frac{1.414 \angle -135^\circ}{1.414 \angle -45^\circ} = 1 \angle -90^\circ.$$

$$\therefore S = \frac{1 + 1}{1 - 1} = \frac{2}{0} = \infty.$$

Example 10.25 An aerial of $(200 - j300) \Omega$ is to be matched with 500Ω lines. The matching is to be done by means of a low loss 600Ω stub line. Find the position and length of the stub line used if the operating wave length is 20 metres.

Solution Given: $Z_R = 200 - j300 \Omega = 360.55 \angle -56.31$, $Z_0 = 500 \Omega$, $\lambda = 20$ m.

We know that the reflection coefficient is

$$K = \frac{Z_R - Z_0}{Z_R + Z_0} = \frac{200 - j300 - 500}{200 - j300 + 500} = \frac{-300 - j300}{700 - j300} = 0.2068 - j0.5172.$$

$$\therefore K = 0.557 \angle -110.8^\circ.$$

So, $|K| = 0.557$ and $\phi = -110.8^\circ$.

We know that the position of the stub line l_s in terms of the reflection coefficient is

$$l_s = \frac{\lambda}{2\pi} (\phi + \pi - \cos^{-1}(|K|)).$$

Substituting the values of λ , ϕ and $|K|$, we get,

$$\begin{aligned} l_s &= \frac{20}{2\pi} (-110.8 + \pi - \cos^{-1}(0.557)) \\ &= \frac{10}{180} (-110.8 + 180 - 56.15) = \frac{10 \times 12.05}{180} = 0.669. \end{aligned}$$

The stub position from the aerial is

$$l_s = 0.669 \text{ metres.}$$

Also the length of the stub line l_s in terms of the reflection coefficient $|K|$ is

$$l_s = \frac{\lambda}{2\pi} \tan^{-1} \frac{\sqrt{1 - |K|^2}}{2|K|}.$$