

Code No: 157EM

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B. Tech IV Year I Semester Examinations, February/March - 2022

**ELECTRIC DRIVES AND CONTROL****(Computer Science and Engineering)**

Time: 3 Hours

Max. Marks: 75

Answer any Five Questions  
All Questions Carry Equal Marks

---

- 1.a) What are the advantages of electric drives to mechanical drives?  
b) With a neat block diagram, explain the different components of an electric drive. [7+8]
- 2.a) What are the functions of a power modulator in an electric drive?  
b) Compare AC drives and DC drives. Discuss factors to be taken into account in selecting an electric drive. [7+8]
- 3.a) Explain the operation of a closed-loop speed control scheme with an inner current control loop. What are the various functions of the inner current control loop?  
b) A 220V, 1200 rpm, 10A separately, excited dc motor is fed from a single-phase full converter with an ac source voltage of 230V, 50Hz. Armature circuit resistance is  $1\Omega$ . The Armature current is continuous. Calculate firing angle for
  - i) rated motor torque at 600 rpm
  - ii) half the rated motor torque at (-600) rpm. [8+7]
- 4.a) What is steady-state stability? What is the condition for the system's steady-state stability with respect to electric drives?  
b) Explain different modes of operation of an electric drive. [8+7]
- 5.a) Explain in detail any one method of electrical braking in DC machines.  
b) Explain the operation of a single-phase full converter fed separately excited DC motor drive. [6+9]
- 6.a) Describe the working of the step-down DC chopper, with the help of a suitable circuit diagram and wave-form diagrams. State the relation between output and input voltages. How is the speed of a DC motor controlled using a step-down chopper?  
b) A 100 V d.c shunt motor has armature resistance and field resistances of 0.4 ohms and 100 ohms respectively. At a particular constant torque load, it takes a current of 25 A at the speed of 1200 r.p.m. A chopper is used to control the speed of the motor. Find  $T_{ON}$  to reduce the speed to 800 r.p.m. at a chopper frequency of 500 Hz. [8+7]
7. Sketch and explain the circuit, using a thyristor controller, to control the speed of a three-phase induction motor by varying the stator voltage. Mention the merits and demerits of this method. Also, sketch and explain the torque-speed characteristics when stator voltage control is used. [15]
8. What are the power factor improvement methods used for energy conservation in drives? Explain in detail any two ways in which it can be achieved. [15]