

Code No: 153AN

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B. Tech II Year I Semester Examinations, March - 2022

DIGITAL SYSTEM DESIGN

(Electronics and Communication Engineering)

Time: 3 Hours

Max. Marks: 75

Answer any five questions  
All questions carry equal marks

- - -

- 1.a) Solve for x  
i)  $(257)_8 = (x)_2$     ii)  $(21.625)_{10} = (x)_8$     iii)  $(BC.2)_{16} = (x)_8$     iv)  $(33)_{10} = (201)_x$
- b) Obtain dual of the following Boolean expressions  
(i)  $AB+A(B+C)+B'(B+D)$     (ii)  $A+B+A'B'C$ .    [8+7]
- 2.a) Express the Decimal Digits 0-9 in BCD, 2421, 84-2-1 and Excess-3.  
b) Using the tabular method, obtain the minimal expression for  
 $F = \sum m(6, 7, 8, 9) + \sum d(10, 11, 12, 13, 14, 15)$ .    [7+8]
- 3.a) Minimize the following expression using K-map and realize using NAND Gates.  
 $F(A,B,C,D) = \sum m(1,3,7,11,15) + \sum d(0,2,5)$ .  
b) Construct a full adder using only two half adders and one OR gate.    [8+7]
- 4.a) With the aid of external logic, convert D type flip-flop to a JK flip-flop.  
b) Design a synchronous modulo-12 counter using JK flip-flop.    [5+10]
- 5.a) Find the characteristic equation for:  
i) T flip-flop    ii) D flip-flop  
b) Draw and explain the operations of 4-bit universal shift register.    [8+7]
- 6.a) Draw and explain the modulo N –counters.  
b) Explain concept of minimal cover table.    [10+5]
- 7.a) Discuss about the approaches of designing synchronous sequential finite state machines.  
b) Design a 1101 sequence detector and draw its logic diagram.    [5+10]
8. Write a short note on followings:  
a) CMOS transmission gate  
b) Tristate TTL  
c) AND, OR gates using DTL.    [5+5+5]