

**R16**

**Code No: 138FY**

**JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD**

**B. Tech IV Year II Semester Examinations, July - 2021**

**ELECTRONIC MEASURING INSTRUMENTS**

**(Common to CE, ME, EIE, MIE)**

**Time: 3 hours**

**Max. Marks: 75**

**Answer any Five Questions  
All Questions Carry Equal Marks**

- - -

- 1.a) The expected value of current through a resistor is 1330mA, but the measurement yields a current value of 1286mA. Calculate the percentage of accuracy and percentage of error.
- b) List out the characteristics of instruments that are used to measure an unvarying process condition. [6+9]
- 2.a) An engineer wants to generate a sawtooth wave that varies in frequency from a fraction of Hertz to several hundred KiloHertz. With a neat block diagram design the device and explain its working.
- b) Draw the block diagram that provides a sinusoidal output voltage whose frequency varies continuously over audio frequency band. [8+7]
- 3.a) Explain how an unknown resistance can be measured when it is connected in series to the D'Arsonval moment.
- b) A CRO is set to a time base of 0.1 ms/cm with a 10cm amplitude. Sketch the display of the pulse signal waveform with a pulse repetition rate of 3000Hz and duty cycle of 30% .[9+6]
- 4.a) An engineer wants to plot the instantaneous relation between two variables  $G = F(s)$ . Explain how plotting of one variable against another variable is done.
- b) Explain the working of Servo transducer and what are the applications of it? [7+8]
- 5.a) Briefly explain the working principles and measurement of force by any two nonelectric techniques?
- b) Describe the method of measuring flow rate with a neat diagram. [8+7]
- 6.a) The accuracy of five digital voltmeters are checked by using each of them to measure a standard 2.0000V from a calibration instrument. The voltmeter readings are as follows:  $V_1=2.001v$ ,  $V_2=2.002v$ ,  $V_3=1.999v$ ,  $V_4=1.998v$  and  $V_5=2.0000v$ . Calculate the average measured voltage and the average deviation
- b) What is the difference between pulse generator and square wave generator? Also discuss requirements of Pulse. [8+7]

- 7.a) Design a multirange ammeter with ranges of 0-100 mA, 0-300 mA, 0-600 mA, 0-2 A employing individual shunts for each range. A D' Arsonval movement with an internal resistance of  $600 \Omega$  and a full scale current of  $200 \mu\text{A}$  is available.
- b) Draw the basic block diagram of an oscilloscope and explain the function of each block. [6+9]
- 8.a) Sketch the DC signal conditioning circuit for pressure measurement using strain gauge. Justify it.
- b) An ac LVDT has the following data: Input = 8.2 V, Output = 4.3 V, range  $\pm 0.3$  in. Determine (i) Calculate the output voltage Vs Core position for a core moment going from + 0.45 in. to - 0.30 in. (ii) The output voltage when the core is -0.25 in. from the centre. [8+7]

--ooOoo--