

Code No: 138AQ

R16

JAWAHARLAL NEHRU TECHNOLOGICAL UNIVERSITY HYDERABAD

B. Tech IV Year II Semester Examinations, July - 2021

ANALOG CMOS IC DESIGN

(Electronics and Communication Engineering)

Time: 3 hours


Max. Marks: 75

**Answer any Five Questions
All Questions Carry Equal Marks**

- - -

- 1.a) Deduce the small signal model for an n-channel MOSFET taking into account the body effect.
- b) Derive an expression for g_m of an N-channel MOS FET operating in linear and saturation regions. [7+8]
- 2.a) Explain how to realize Resistor using Active devices.
- b) Consider a source follower which is biased by a current mirror. The dimensions of all the transistors are $100\mu\text{m}/1.6\mu\text{m}$, $\mu_n C_{ox} = 90\mu\text{A}/\text{V}^2$, $\mu_p C_{ox} = 30\mu\text{A}/\text{V}^2$, $I_{bias} = 100\mu\text{A}$, $\gamma_n = 0.5\text{V}^{1/2}$, $r_{dx-n} = 8000L(\mu\text{m})/I_D(\text{mA})$. What is the gain of the stage? [7+8]
- 3.a) Explain how power-supply sensitivity can be reduced in bootstrap bias technique.
- b) Design a second order Butterworth low pass filter with a cutoff frequency of 500 Hz and a pass band gain of -2. Assume that a $5\text{V} \pm$ power supply and a CMOS clock are used. [7+8]
- 4.a) Why is emitter resistor R_E replaced by a constant current bias circuit in differential amplifier stage of an op-AMP? Explain.
- b) Design the dual input balanced output differential amplifier with the current mirror bias according to the following specifications:
 - i) Supply voltage $V_s = \pm 12\text{V}$
 - ii) Maximum output voltage swing – 7Vpp. [7+8]
5. Discuss in detail the compensation of OP amp that makes it completely independent of process and temperature variations. [15]
- 6.a) With neat sketch and necessary equations explain the design aspect of a two-stage open loop comparator for slewing response.
- b) Give an account of charge injection errors in connection with comparators and suggest a method to minimize the same. [7+8]

 - 7.a) Explain about the Bipolar simple current mirror with degeneration helper with necessary equations.
- b) Determine the DC gain and 3-dB bandwidth frequency for the circuit with the load impedance of $150\text{k}\Omega \parallel 20\text{pF}$ added to the output. [7+8]



8. Choose values of $V_{GS} = 1, 2, 3, 4$ and 5V , assume that the channel modulation parameter is zero. Sketch to scale the output characteristics of an enhancement n-channel device if $V_T = 0.7\text{V}$ and $I_D = 500\mu\text{A}$ when $V_{GS} = 5\text{V}$ in saturation. [15]

--ooOoo--